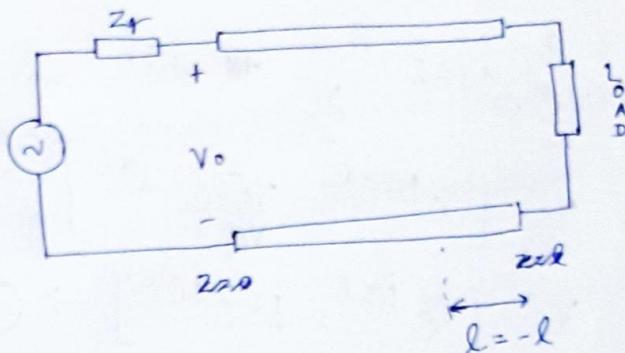


POWER
The transmission line is used in transferring power from source to the load

consider the transmission line



In general

$$V_{S(z)} = V_0^+ e^{-jz} + V_0^- e^{+jz}$$

For a lossless line $\alpha=0$

$$V_{S(z)} = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

[Because it is measured from load]

$$\text{At } z = -l \quad V_{S(-l)} = V_0^+ e^{-j\beta(-l)} + V_0^- e^{+j\beta(-l)}$$

$$V_{S(-l)} = V_0^+ e^{-j\beta(-l)} + V_0^- e^{+j\beta(-l)}$$

$$V_{S(-l)} = V_0^+ e^{+j\beta l} + V_0^- e^{-j\beta l}$$

$$V_{S(-l)} = V_0^+ \left[e^{+j\beta l} + \frac{V_0^-}{V_0^+} e^{-j\beta l} \right]$$

$$V_{S(-l)} = V_0^+ \left[e^{+j\beta l} + R e^{-j\beta l} \right] \rightarrow ①$$

R = Reflection coefficient

$$I_s(z) = \frac{V_o^+ e^{-jz}}{Z_0} - \frac{V_o^- e^{+jz}}{Z_0}$$

(31)

$$\alpha' = 0$$

$$I_s(z) = \frac{V_o^+ e^{-jBz}}{Z_0} - \frac{V_o^- e^{+jBz}}{Z_0}$$

$$z = -l$$

$$I_s(l) = \frac{V_o^+ e^{+j\beta l}}{Z_0} - \frac{V_o^- e^{-j\beta l}}{Z_0}$$

$$I_s(l) = \frac{V_o^+}{Z_0} \left[e^{+j\beta l} - \frac{V_o^-}{V_o^+} e^{-j\beta l} \right]$$

$$I_s(l) = \frac{V_o^+}{Z_0} \left[e^{j\beta l} - r^* e^{-j\beta l} \right] \rightarrow (2)$$

$$P_{ave} = \frac{1}{2} \operatorname{Re} [V_s(z) I_s^*(l)]$$

$$P_{ave} = \frac{1}{2} \operatorname{Re} \left[V_o^+ \left[e^{j\beta l} + r^* e^{-j\beta l} \right] \cdot \left(\frac{V_o^+}{Z_0} \right)^* \left[e^{-j\beta l} - r^* e^{+j\beta l} \right] \right]$$

$$= \frac{1}{2} \operatorname{Re} \left[\frac{|V_o^+|^2}{Z_0} \left[1 - |r^*|^2 + r^* e^{-j2\beta l} - r^{*+} e^{j2\beta l} \right] \right]$$

since Last two terms are imaginary

$$P_{ave} = \frac{1}{2 Z_0} \left[|V_o^+|^2 (1 - |r^*|^2) \right]$$

$$P_{ave} = \frac{|V_o^+|^2}{2 Z_0} (1 - (|r^*|^2))$$

$$\boxed{P_{ave} = \frac{|V_o^+|^2}{2 Z_0} \left[1 - |r^*|^2 \right]} \rightarrow (3)$$

(32)

We know $P_t = P_i - P_r$

P_t = Transmitted power

P_i = Incident Power

P_r = Reflected power

From Equation (3) it is evident that the power is constant and it does not depend on "l".

When $\Gamma = 0$, Maximum power is transmitted

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{when } Z_L = Z_0 \quad \Gamma_L = 0$$

Reflection coefficient for different cases of lossless line
There are three different cases they are

a) Shorted Line ($Z_L = 0$)

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{0 - Z_0}{0 + Z_0} = -1$$

$$S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} = \frac{1 + 1}{1 - 1} = \infty$$

$$Z_{sc} = Z_{in} \Big|_{Z_L=0} = Z_0 \left[\frac{Z_L^0 + j Z_0 \tan \beta l}{Z_0 + j Z_L^0 \tan \beta l} \right]$$

$$Z_{sc} = Z_{in} \Big|_{Z_L=0} = j Z_0 \tan \beta l$$

$$T = \frac{1 + \Gamma}{1 - \Gamma}$$

B) Open circuited Line ($Z_L = \infty$)

(33)

$$P_L^c = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{\cancel{Z_L} [1 - \frac{Z_0}{\cancel{Z_L}}]}{\cancel{Z_L} [1 + \frac{Z_0}{\cancel{Z_L}}]} = 1$$

$$S = \frac{1 + |P_L^c|}{1 - |P_L^c|} = \frac{1 + 1}{1 - 1} = \infty$$

$$\begin{aligned} Z_{oc} &= \lim_{Z_L \rightarrow \infty} Z_{in} = \lim_{Z_L \rightarrow \infty} Z_0 \left[\frac{\cancel{Z_L} + j Z_0 \tan \beta l}{\cancel{Z_0} + j Z_L \tan \beta l} \right] \\ &= \lim_{Z_L \rightarrow \infty} Z_{in} = Z_0 \times \frac{Z_0}{Z_0} \left[\frac{1 + j \frac{Z_0}{Z_L} \tan \beta l}{\frac{Z_0}{Z_L} + j \tan \beta l} \right] \\ &= \lim_{Z_L \rightarrow \infty} Z_{in} = Z_0 \left[\frac{1}{j \tan \beta l} \right] \\ &= -j Z_0 \cot \beta l \end{aligned}$$

c) Matched Line ($Z_L = Z_0$)

$$P_L^c = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{Z_L - Z_L}{Z_L + Z_L} = 0 \quad \text{where } d=0$$

$$Z_{in} = Z_0 \left[\frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right]$$


$$Z_{in} = Z_0 \left[\frac{Z_0 + j Z_0 \tan \beta l}{Z_0 + j Z_0 \tan \beta l} \right] = Z_0$$

$$Z_{in} = Z_0$$


$$S = \frac{1 + |P_L^c|}{1 - |P_L^c|} = 1$$

$$Z_{SC} = j z_0 \tan \beta l$$

(34)

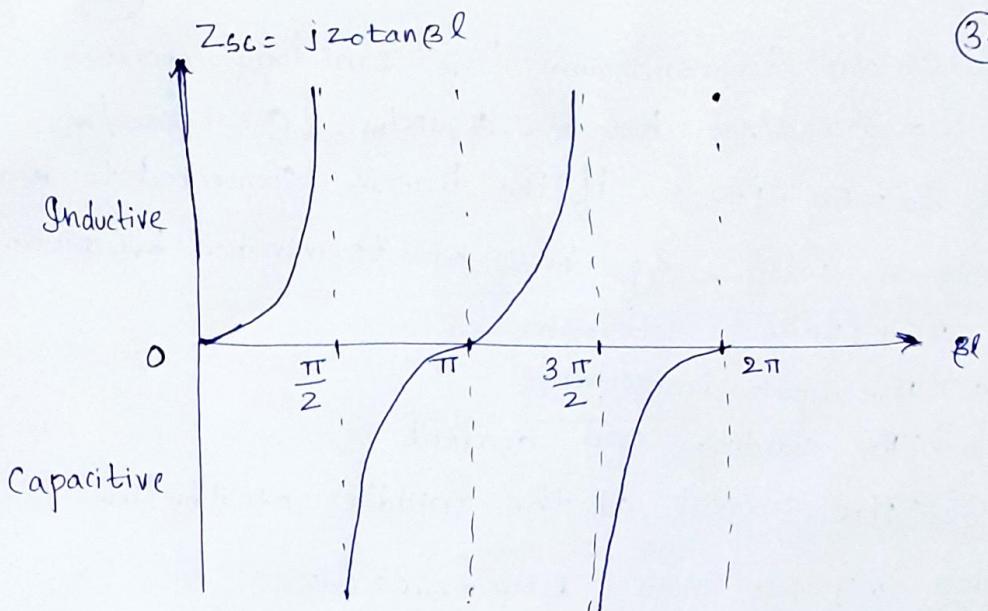

$$Z_{OC} = -j z_0 \cot \beta l$$

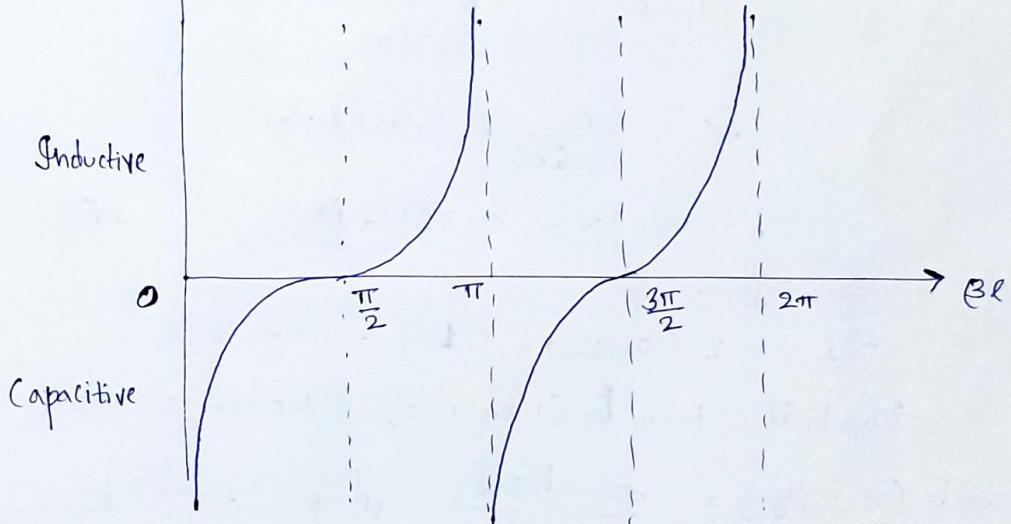

(35)

1) A certain transmission line 2m long operates at $\omega = 10^6 \text{ rad/sec}$ has $\alpha = 8 \text{ dB/m}$, $\beta = 1 \text{ rad/m}$, and $Z_0 = 60 + j40 \Omega$. If the line is connected to a source of $10 \angle 0^\circ$, $Z_g = 40 \Omega$ and terminated by a load of $20 + j50 \Omega$, determine

- (a) The input impedance
- (b) The sending end current

- (c) The current at the middle of the line

Solution: (a) We know $1 \text{ NP} = 8.686 \text{ dB}$

$$\alpha = 8 \text{ dB/m}$$

$$1 \text{ NP} - 8.686 \text{ dB}$$

$$? - 8 \text{ dB}$$

$$\alpha = \frac{8}{8.686} = 0.921 \text{ NP/m}$$

$$\gamma = \alpha + j\beta = 0.921 + j1 \quad (\beta = 1)$$

$$l = 2$$

$$\gamma l = 2(0.921 + j1) = 1.84 + j2$$

$$\tanh \gamma l = \tanh (1.84 + j2) = 1.033 - j0.03929$$

$$\tanh(\alpha \pm jy) = \frac{\sinh 2x}{\cosh 2x + \cos 2y} \pm j \frac{\sinh 2y}{\cosh 2x + \cos 2y}$$

$$Z_{in} = Z_0 \left[\frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} \right]$$

$$= (60 + j40) \left[\frac{(20 + j50) + (60 + j40)(1.033 - j0.03929)}{(60 + j40) + (20 + j50)(1.033 - j0.03929)} \right]$$

$$Z_{in} = 60.25 + j38.49 \Omega = 71.66 \angle 32.77^\circ$$

(36)

b) The sending end current

$$I(z=0) = I_0$$

$$I(z=0) = \frac{V_g}{Z_{in} + Z_g} = \frac{10}{60.25 + j38.79 + 40}$$

$$I(z=0) = 93.03 \angle -21.15^\circ \times 10^{-3} A$$

c) To find the current at any point, we need V_o^+ and V_o^-

$$I_0 = I(z=0) = 93.03 \angle -21.15^\circ \times 10^{-3}$$

$$V_o = Z_{in} I_0 = (f1.66 \angle 32.7^\circ)(93.03 \times 10^{-3} \angle -21.15^\circ)$$

$$V_o = 6.68 \angle 11.62^\circ$$

$$\text{We know } V_o^+ = \frac{1}{2} [V_o + I_o Z_o]$$

$$= \frac{1}{2} [6.68 \angle 11.62^\circ + [93.03 \times 10^{-3} \angle -21.15^\circ] [60 + j40]]$$

$$= 6.68 \angle 12.08^\circ$$

$$V_o^- = \frac{1}{2} [V_o - I_o Z_o]$$

$$= 0.0518 \angle 260^\circ$$

At the middle of the line, $z = l/2$,

$$\gamma z = 0.921 + j1$$

$$I_s(z=l/2) = \frac{V_o^+}{Z_o} e^{-\gamma z} - \frac{V_o^-}{Z_o} e^{+\gamma z}$$

$$I_s(z=l/2) = 35.10 \angle 281^\circ \times 10^{-3} A$$

Note: Velocity is generally termed as phase velocity

(46)

- ① A transmission line operating at 500 MHz has $Z_0 = 80 \Omega$, $\alpha = 0.04 \text{ NP/m}$, $\beta = 1.5 \text{ rad/m}$. Find the line parameters R , L , G and C

Solution: Since $\alpha = 0.04 \text{ NP/m} \neq 0$ and $Z_0 = 80 \Omega$, which is real, the given transmission line is a distortionless transmission line.

$$\therefore RC = GL \rightarrow ①$$

$$\alpha = \sqrt{RG} \rightarrow ②$$

$$\beta = \omega \sqrt{LC} \rightarrow ③$$

$$\text{But } C = \frac{GL}{R} \rightarrow ④$$

$$\text{using } ④ \text{ in } ③ \quad \beta = \omega \sqrt{\frac{L \times GL}{R}}$$

$$\beta = \omega L \sqrt{\frac{G}{R}} \rightarrow ⑤$$

$$\text{But we know for a distortion less line } Z_0 = \sqrt{\frac{L}{C}} \rightarrow ⑥$$

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{R}{G}} = 80 \rightarrow ⑦$$

$$\beta = \omega L \times \frac{1}{\sqrt{\frac{R}{G}}} \Rightarrow \frac{\omega L}{Z_0} = \beta \rightarrow ⑧$$

$$\text{consider } \alpha = \sqrt{RG} \rightarrow ② \quad Z_0 = \sqrt{\frac{R}{G}} \rightarrow ⑦$$

$$\alpha Z_0 = \sqrt{RG} \times \sqrt{\frac{R}{G}} = R$$

$$0.04 \times 80 = R \Rightarrow R = 3.2 \Omega/\text{m}$$

(47)

We know $Z_0 = \sqrt{\frac{R}{G}} \Rightarrow Z_0^2 = \frac{R}{G}$

$$G = \frac{R}{Z_0^2} = \frac{3.2}{80 \times 80} = 5 \times 10^{-4} \text{ S/m}$$

$$\boxed{G = 5 \times 10^{-4} \text{ S/m}}$$

From (8) $\frac{\omega L}{Z_0} = \beta \Rightarrow L = \frac{Z_0 \beta}{\omega}$

$$L = \frac{80 \times 1.5}{2\pi \times f} = \frac{80 \times 1.5}{2\pi \times 500 \times 10^6} = 38.2 \times 10^{-9} \text{ H}$$

$$\boxed{L = 38.2 \times 10^{-9} \text{ H/m}}$$

$$RC = GL \Rightarrow C = \frac{GL}{R}$$

$$C = \frac{5 \times 10^{-4} \times 38.2 \times 10^{-9}}{3.2} = 5.968 \times 10^{-12} \text{ F/m}$$

$$\boxed{C = 5.968 \times 10^{-12} \text{ F/m}}$$

② A telephone line has $R = 30 \Omega/\text{km}$, $L = 100 \text{mH/km}$, $G = 0$ and $C = 20 \mu\text{F/km}$. At $f = 1 \text{kHz}$ obtain

- (a) The characteristic impedance of the line
- (b) The propagation constant
- (c) The phase velocity

Solution: Given $R = 30 \times 10^{-3} \Omega/\text{m}$ $L = 100 \times 10^{-3} \times 10^{-3} \text{ H/m}$,
 $G = 0 \text{ v/m}$ $C = 20 \times 10^{-6} \times 10^{-3} \text{ F/m}$

$$\begin{aligned} (a) Z_0 &= \sqrt{\frac{R + j\omega L}{G + j\omega C}} \\ &= \sqrt{\frac{30 \times 10^{-3} + j2\pi \times 1 \times 10^3 \times 100 \times 10^{-6}}{0 + j2\pi \times 1 \times 10^3 \times 20 \times 10^{-6} \times 10^{-3}}} \\ &= 70.73 - j1.688 = 70.75 \angle -1.367^\circ \Omega \end{aligned}$$

$$\begin{aligned} (b) \gamma &= \sqrt{(R + j\omega L)(G + j\omega C)} \\ \gamma &= \sqrt{(30 \times 10^{-3} + j2\pi \times 10^3 \times 100 \times 10^{-6})(0 + j2\pi \times 10^3 \times 20 \times 10^{-9})} \\ \gamma &= 2.121 \times 10^{-4} + j8.888 \times 10^{-3} / \text{m} \end{aligned}$$


$$(c) \text{The phase velocity } u = \frac{\omega}{\beta} = \frac{2\pi \times 10^3}{8.888 \times 10^{-3}}$$

$$u = 7.069 \times 10^5 \text{ m/s}$$

Note: (i) Velocity is generally termed as phase Velocity

(49)

- 3) The transmission line shown in figure is 40m long and has $V_g = 15 \angle 0^\circ$ V_{rms}, $Z_0 = 30 + j60 \Omega$ and $V_L = 5 \angle -48^\circ$ V_{rms}. If the line is matched to the load, calculate
- (a) The input impedance Z_{in}
 - (b) The sending-end current I_{in} and voltage V_{in}
 - (c) The propagation constant.

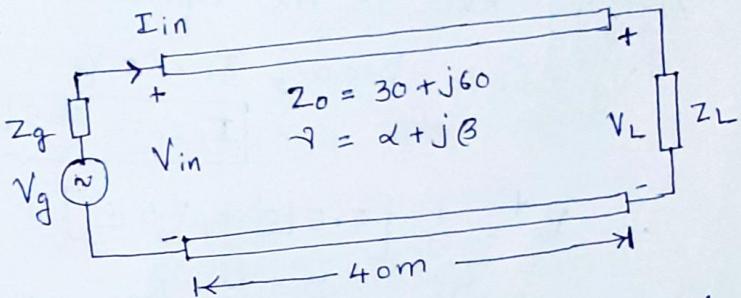Solution :-

- (a) Given that transmission line is matched

$$\therefore Z_0 = Z_L = 30 + j60 \Omega$$

$$\therefore Z_{in} = Z_0 = 30 + j60 \Omega$$

(b) $V_{in} = V_0 = \frac{Z_{in}}{Z_{in} + Z_g} V_g = \frac{Z_0 V_g}{Z_0 + Z_g}$ Because $Z_{in} = Z_0$
 $Z_g = Z_0$

$$V_{in} = \frac{V_g}{2} = \frac{15 \angle 0^\circ}{2} = 7.5 \angle 0^\circ \text{ V}_{rms}$$

$$I_{in} = I_0 = \frac{V_g}{Z_g + Z_{in}}$$
 Since the line is matched
 $Z_g = Z_0 \quad Z_{in} = Z_0$


$$I_{in} = I_0 = \frac{V_g}{Z_0 + Z_0} = \frac{15 \angle 0^\circ}{2(Z_0)} = \frac{15 \angle 0^\circ}{2(30 + j60)}$$

$$= 0.1118 \angle -63.43^\circ$$



$$m/24 \quad 1010.8 = \frac{(2.1) \times 2}{0.4}$$

(50)

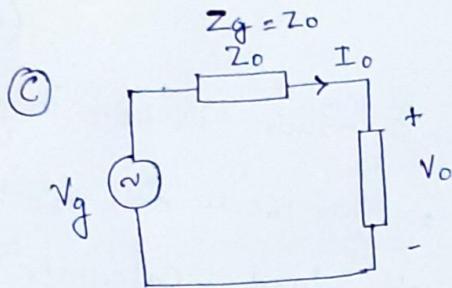

Consider the equivalent circuit as shown in figure

since line is matched

$$Z_0 = Z_L \Rightarrow \Gamma = 0 \Rightarrow V_0^- = 0$$

We know $V_0^+ = \frac{1}{2} [V_0 + I_0 Z_0]$

$$\left\{ \begin{array}{l} V_{S(z)} = V_0 = V_0^+ + V_0^- \\ I_{S(z)} = I_0 = \frac{V_0^+ - V_0^-}{Z_0} \end{array} \right.$$

$$V_0 = 7.5 \angle 0^\circ$$

Applying KVL to the equivalent circuit

$$V_g - I_0 Z_0 - V_0 = 0, \quad I_0 Z_0 = V_g - V_0 = 15 \angle 0^\circ - 7.5 \angle 0^\circ$$

$$\boxed{I_0 Z_0 = 7.5 \angle 0^\circ}$$

$$\therefore V_0^+ = \frac{1}{2} [7.5 \angle 0^\circ + 7.5 \angle 0^\circ] = 7.5 \angle 0^\circ$$

$$V_L = V_0 e^{-j\alpha l} + V_0 e^{+j\alpha l} \quad [\text{Because } \Gamma = 0]$$

$$\frac{V_L}{V_0^+} = e^{-j\alpha l} \Rightarrow e^{+j\alpha l} = \frac{V_0^+}{V_L} = \frac{7.5 \angle 0^\circ}{5 \angle -48^\circ}$$

$$\therefore e^{+j\alpha l} = 1.5 \angle 48^\circ \Rightarrow e^{(\alpha + j\beta)l} = 1.5 \angle 48^\circ$$

$$e^{\alpha l} e^{j\beta l} = 1.5 e^{j48^\circ} \rightarrow \textcircled{1}$$

Equating real components

$$e^{\alpha l} = 1.5$$

Taking Natural log on both sides

$$\alpha l = \ln(1.5)$$

$$\alpha = \frac{\ln(1.5)}{l} \quad \text{where } l = 40$$

$$\alpha = \frac{\ln(1.5)}{40} = 0.0101 \text{ NP/m}$$

(51)

Equating imaginary components

$$e^{j\beta l} = e^{j48^\circ}$$

Converting degrees into radians

$$\left(\frac{\pi}{180}\right)^\circ = \frac{180^\circ}{48^\circ}$$

$$e^{j\beta l} = e^{j\frac{48^\circ \times \pi}{180}}$$

$$\beta l = \frac{48^\circ \times \pi}{180}$$

$$\beta = \frac{1}{l} \times \frac{48^\circ \times \pi}{180^\circ} = \frac{1 \times 48^\circ \times \pi}{40 \times 180^\circ}$$

$$\beta = 0.02094 \text{ rad/m}$$

$$\gamma = \alpha + j\beta$$

$$\gamma = 0.0101 + j0.02094 / \text{m}$$

length of
the tr line
[∴ $l = 40 \text{ m}$]

4) a) show that at high frequencies ($R \ll \omega L$, $G \ll \omega C$) (52)

$$\gamma = \left(\frac{R}{2} \sqrt{\frac{C}{L}} + \frac{G}{2} \sqrt{\frac{L}{C}} \right) + j\omega \sqrt{LC}$$

b) obtain a similar formula for z_0

solution:

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$\gamma = j\omega \sqrt{LC} \sqrt{\left(1 + \frac{R}{j\omega L}\right)\left(1 + \frac{G}{j\omega C}\right)}$$

$$\gamma = j\omega \sqrt{LC} \sqrt{1 - \frac{RG}{\omega^2 LC} + \frac{R}{j\omega L} + \frac{G}{j\omega C}}$$

$\frac{RG}{\omega^2 LC}$ is very small and it can be neglected

Because $R \ll \omega L$ and $G \ll \omega C$

$$\gamma \approx j\omega \sqrt{LC} \sqrt{1 + \frac{R}{j\omega L} + \frac{G}{j\omega C}}$$

$$= j\omega \sqrt{LC} \sqrt{1 + \frac{1}{j} \left(\frac{R}{\omega L} + \frac{G}{\omega C} \right)}$$

$$\gamma = j\omega \sqrt{LC} \left(1 + \frac{1}{j} \left(\frac{R}{\omega L} + \frac{G}{\omega C} \right) \right)^{1/2}$$

Applying Binomial theorem to the term $\left[1 + \frac{1}{j} \left(\frac{R}{\omega L} + \frac{G}{\omega C} \right) \right]^{1/2}$ we get

$$\gamma = j\omega \sqrt{LC} \left[1 + \frac{1}{2j} \left(\frac{R}{\omega L} + \frac{G}{\omega C} \right) + \dots \right]$$

Higher order terms of Binomial theorem expansion are neglected.

$$\omega = j\omega\sqrt{LC} \left[1 + \frac{R}{2j\omega L} + \frac{G}{2j\omega C} \right]$$

$$\omega = \frac{j\sqrt{LC} \times R}{2j\omega L} + \frac{j\sqrt{LC} \cdot G}{2j\omega C} + j\omega\sqrt{LC}$$

$$\boxed{\omega = \left(\frac{R}{2} \sqrt{\frac{C}{L}} + \frac{G}{2} \sqrt{\frac{L}{C}} \right) + j\omega\sqrt{LC}}$$

(b)

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{L}{C}} \sqrt{\frac{(1+\frac{R}{j\omega L}) \times j\omega}{(1+\frac{G}{j\omega C}) \times j\omega}}$$

$$Z_0 = \sqrt{\frac{L}{C}} \left(1 + \frac{R}{j\omega L}\right)^{1/2} \left(1 + \frac{G}{j\omega C}\right)^{-1/2}$$

Applying Binomial theorem

$$Z_0 = \sqrt{\frac{L}{C}} \left[1 + \frac{R}{2j\omega L}\right] \left[1 - \frac{G}{2j\omega C}\right]$$

Higher order terms of Binomial theorem are neglected.

$$Z_0 = \sqrt{\frac{L}{C}} \left[1 + \frac{R}{j^2\omega^2 L} - \frac{G}{2j\omega C} - \frac{RG}{4j^2\omega^2 LC} \right]$$

$$Z_0 \approx \sqrt{\frac{L}{C}} \left[1 - \frac{jR}{2\omega L} + \frac{jG}{2\omega C}\right]$$

$$\boxed{Z_0 \approx \sqrt{\frac{L}{C}} \left[1 + j \left(\frac{G}{2\omega C} - \frac{R}{2\omega L}\right)\right]}$$

(55)

1) on a distortionless line, the voltage wave is given by

$$V(l') = 120 e^{j0.0025l'} \cos(10^8 t + 2l') + 60 e^{-j0.0025l'} \cos(10^8 t - 2l')$$

where l' is the distance from the load.


If $Z_L = 300 \Omega$, find (a) α , β and u (b) Z_0 and $I(l')$

Solution: We know that

$$(a) V(z, t) = \operatorname{Re} [V_s(z) e^{j\omega t}]$$

$$V(z, t) = V_o^+ e^{-\alpha z} \cos(\omega t - \beta z) + V_o^- e^{+\alpha z} \cos(\omega t + \beta z) \quad (1)$$

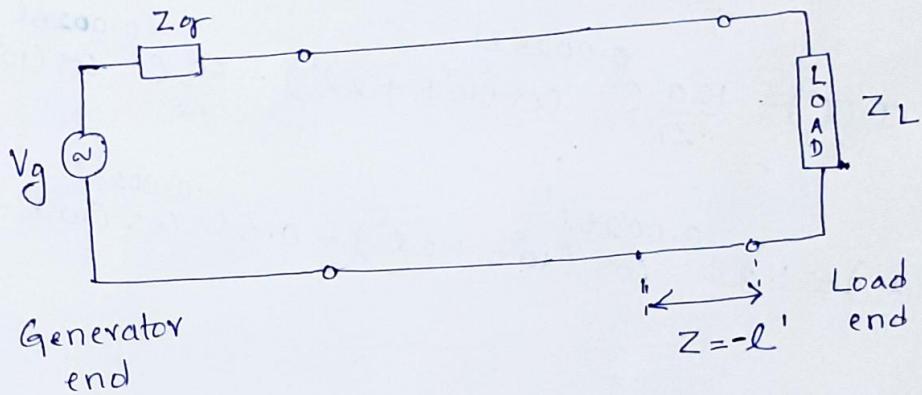where z = distance measured from the generator end



In the given problem l' is the distance from the load. Therefore equation (1) becomes (2)

by substituting $z = -l'$

$$\therefore V(l') = V_o^+ e^{-\alpha(-l')} \cos(\omega t - \beta(-l')) + V_o^- e^{+\alpha(-l')} \cos(\omega t + \beta(-l'))$$

$$\therefore V(l') = V_o^+ e^{+\alpha l'} \cos(\omega t + \beta l') + V_o^- e^{-\alpha l'} \cos(\omega t - \beta l') \rightarrow (2)$$

$$\therefore V(l') = 120 e^{j0.0025l'} \cos(10^8 t + 2l') + 60 e^{-j0.0025l'} \cos(10^8 t - 2l') \rightarrow (3)$$

Comparing (2) and (3) we get

(56)

$$V_0^+ = 120, V_0^- = 60, \alpha = 0.0025, \beta = 2, \omega = 10^8 \text{ rad/sec}$$

$$\therefore \alpha = 0.0025 \text{ Np/m}$$

$$\beta = 2 \text{ rad/m}$$

$$u = \frac{\omega}{\beta} = \frac{10^8}{2} = 0.5 \times 10^8 \text{ m/s}$$

(b)

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{60}{120} = 0.5$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} \Rightarrow 0.5 = \frac{300 - Z_0}{300 + Z_0}$$

$$\therefore Z_0 = 100 \Omega$$

$$I(l') = \frac{120}{Z_0} e^{0.0025l'} \cos(10^8 t + 2l') - \frac{60}{Z_0} e^{-0.0025l'} \cos(10^8 t - 2l')$$

$$I(l') = 1.2 e^{0.0025l'} \cos(10^8 t + 2l') - 0.6 e^{-0.0025l'} \cos(10^8 t - 2l') A$$

⑧ bns ⑨ prinqwss

(57)

2) A distortionless cable is 4m long and has a characteristic impedance of 60Ω . An attenuation of 0.24 dB is observed at the receiving end.

Also, a signal applied to the cable is delayed by $80\mu s$ before is measured at the receiving end. Find R, G, L and C for the cable

Solution: For a distortionless cable

$$RC = LG \rightarrow ①$$

$$Z_0 = \sqrt{\frac{L}{C}} = 60 \rightarrow ②$$

$$\text{phase velocity } u = \frac{\omega}{B} = \frac{1}{\sqrt{LC}} = \frac{\text{length}}{\text{time}} = \frac{4}{80 \times 10^{-6}}$$

$$\frac{1}{\sqrt{LC}} = \frac{4}{80 \times 10^{-6}} \rightarrow ③$$

$$② \times ③ \quad \sqrt{\frac{L}{C}} \times \frac{1}{\sqrt{LC}} = \frac{60 \times 4}{80 \times 10^{-6}}$$

$$\frac{1}{C} = \frac{60 \times 4}{80 \times 10^{-6}}$$

$$C = 333.33 \text{ nF/m}$$

$$Z_0 = \sqrt{\frac{L}{C}} = 60$$

$$\frac{L}{C} = 60 \times 60$$

$$L = 60 \times 60 \times 333.33 \times 10^{-9}$$

$$L = 1.20 \times 10^{-3} \text{ H/m}$$

$$\alpha l = 0.24 \text{ dB}$$

$$\alpha l = \frac{0.24}{8.686}$$

meters per m
and 1 NP - 8.686 dB
0.24 dB

$$\alpha l = 0.0276 \text{ NP}$$

$$\alpha = \text{and } \frac{0.0276}{l} = \frac{0.0276}{4} = 6.9 \times 10^{-3}$$

$$\alpha = \sqrt{RG} \quad \alpha^2 = RG$$

$$RG = (6.9 \times 10^{-3})^2 \rightarrow ④$$

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{R}{G}} = 60 \quad \left\{ \begin{array}{l} \frac{R}{L} = \frac{G}{C} \\ \frac{R}{G} = \frac{L}{C} \end{array} \right.$$

$$\frac{R}{G} = 60 \times 60 \rightarrow ⑤$$

$$④ \times ⑤ \quad R^2 = (6.9 \times 10^{-3})^2 \times 60 \times 60$$

$$R = 0.414 \Omega/\text{m}$$

$$\alpha = \sqrt{RG}$$

$$\alpha^2 = RG$$

$$G = \frac{\alpha^2}{R} = \frac{(6.9 \times 10^{-3})^2}{0.414} = 115 \times 10^{-6} \text{ S/m}$$

$$115 \times 10^{-6} \times 0.2 \times 0.2 = 1$$

$$115 \times 10^{-6} \times 0.2 \times 0.1 = 1$$

- 3) A coaxial line 5.6m long has distributed parameter $R = 6.5 \Omega/m$, $L = 3.4 \mu H/m$, $G = 8.4 mS/m$ and $C = 21.5 pF/m$. If the line operates at 2MHz, calculate the characteristic impedance and the end to end propagation time delay.

Solution : $R + j\omega L = 6.5 + j2\pi \times 2 \times 10^6 \times 3.4 \times 10^{-6}$
 $= 6.5 + j42.73 = 43.22 \angle 81.35^\circ$

$$G + j\omega C = 8.4 \times 10^{-3} + j2\pi \times 2 \times 10^6 \times 21.5 \times 10^{-12}$$
 $= (8.4 + j0.2701) \times 10^{-3} = 8.404 \times 10^{-3} \angle 1.84^\circ$

$$Z_0 = \sqrt{\frac{43.22 \angle 81.35}{8.404 \times 10^{-3} \angle 1.84}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$Z_0 = 71.71 \angle 39.75^\circ$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\gamma = \sqrt{43.22 \angle 81.35^\circ \times 8.404 \times 10^{-3} \angle 1.84}$$

$$\gamma = 0.6026 \angle 41.595$$

$$\gamma = 0.4506 + j0.3999 /m$$

$$\alpha = 0.4506 \quad \beta = 0.3999$$


~~distance~~ γ ~~velocity~~ = $\frac{\text{distance}}{\text{time}}$

$$\text{time} = \frac{\text{distance}}{\text{velocity}} = \frac{\text{End} - \text{start}}{\text{average}} = \frac{5.6}{u}$$

$$\text{time} = \frac{5.6}{\frac{u}{\beta}} = \frac{\beta \times 5.6}{2\pi \times 2 \times 10^6} = \frac{0.3999 \times 5.6}{2 \times \pi \times 2 \times 10^6}$$
 $= 0.1782 \mu\text{sec}$

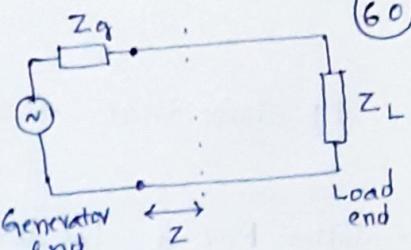(60)

Transmission Line Equations - (Additional)



Consider $\frac{d^2 V_s}{dz^2} - \gamma^2 V_s = 0$

The solution to above linear homogeneous

differential equation is
 $V_s(z) = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z}$

Where V_o^+ and V_o^- are wave amplitudes
 The instantaneous expression for voltage is

$$V(z, t) = \operatorname{Re}[V_s(z) e^{j\omega t}]$$

$$V(z, t) = V_o^+ e^{-\alpha z} \cos(\omega t - \beta z) + V_o^- e^{+\alpha z} \cos(\omega t + \beta z)$$

Similarly $\frac{d^2 I_s}{dz^2} - \gamma^2 I_s = 0$

The solution to above linear homogeneous differential equation is
 $I_s(z) = I_o^+ e^{-\gamma z} + I_o^- e^{+\gamma z}$

Where I_o^+ and I_o^- are wave amplitudes

The instantaneous expression for current is

$$I(z, t) = \operatorname{Re}[I_s(z) e^{j\omega t}]$$

$$I(z, t) = I_o^+ e^{-\alpha z} \cos(\omega t - \beta z) + I_o^- e^{+\alpha z} \cos(\omega t + \beta z)$$

$$I(z, t) = \frac{V_o^+}{Z_0} e^{-\alpha z} \cos(\omega t - \beta z) - \frac{V_o^-}{Z_0} e^{+\alpha z} \cos(\omega t + \beta z)$$

The second term in the above equation is

negative because $Z_0 = \frac{V_o^+}{I_o^+} = -\frac{V_o^-}{I_o^-}$

In all the above expressions "z" is measured from generator end as shown in figure above.

① show that for a lossless line

$$Z_{sc} Z_{oc} = Z_0^2$$

(61)

Solution: For a lossless line when $Z_L = 0$

$$Z_{sc} = Z_{in} \Big|_{Z_L=0} = j Z_0 \tan \beta l$$

For a lossless line when $Z_L = \infty$

$$Z_{oc} = \lim_{Z_L \rightarrow \infty} Z_{in} = -j Z_0 \cot \beta l$$

$$\begin{aligned} Z_{sc} \times Z_{oc} &= j Z_0 \tan \beta l \times -j Z_0 \cot \beta l \\ &= -j^2 Z_0^2 \quad (1) \end{aligned}$$

$$Z_{sc} \times Z_{oc} = Z_0^2$$

(62)

2) Show that a transmission coefficient may be

defined as $\Gamma_L = \frac{V_L}{V_0^+} = 1 + \Gamma_L' = \frac{2Z_L}{Z_L + Z_0}$

where Γ_L' = Transmission coefficient

Γ_L' = Reflection coefficient.

Solution:

$$\Gamma_L' = \frac{V_L}{V_0^+} = \frac{I_L Z_L}{\frac{1}{2} [V_L + Z_0 I_L]}$$

$$= \frac{I_L Z_L}{\frac{1}{2} [I_L Z_L + Z_0 I_L]}$$

$$= \frac{2 I_L Z_L}{I_L Z_L + I_L Z_0}$$

$$= \frac{2 Z_L}{Z_L + Z_0} \rightarrow (1)$$

$$1 + \Gamma_L' = 1 + \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{2 Z_L}{Z_L + Z_0} \rightarrow (2)$$

$$(1) = (2)$$

$$\Gamma_L' = 1 + \Gamma_L' = \frac{2 Z_L}{Z_L + Z_0}$$

(P1)

- ① Two voltage waves having equal amplitudes frequencies and amplitudes propagate in opposite directions on a lossless transmission line. Determine the total voltage as a function of time and position

Solution: Since the waves have the same frequency we can write their combination using their phasor forms: Assuming phase constant β and real amplitude V_0 , the two wave voltages combine in this way

$$V_{ST}(z) = V_0 e^{-j\beta z} + V_0 e^{+j\beta z}$$

$$= 2V_0 \cos(\beta z)$$

In the real instantaneous form, this becomes

$$V(z, t) = \operatorname{Re} \{ 2V_0 \cos(\beta z) e^{j\omega t} \}$$

$$= 2V_0 \cos(\beta z) \cos(\omega t)$$

This represents a standing wave, in which the amplitude varies as $\cos(\beta z)$ and oscillates in time as $\cos(\omega t)$

(P2)

- 2) A lossless transmission line is 80cm long and operates at a frequency of 600 MHz. The line parameters are $L = 0.25 \mu\text{H/m}$, $C = 100 \text{ pF/m}$. Find the characteristic impedance, the phase constant and the velocity.

Solution: Since the line is lossless

$$R = G = 0$$

The characteristic Impedance

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{0.25 \times 10^{-6}}{100 \times 10^{-12}}} = 50 \Omega$$

$$\text{Since } \gamma = \alpha + j\beta = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$\gamma = \alpha + j\beta = j\omega\sqrt{LC}$$

$$\beta = \omega\sqrt{LC}$$

Phase
constant

$$\beta = 2\pi (600 \times 10^6) \sqrt{0.25 \times 10^{-6} \times 100 \times 10^{-12}}$$

$$\beta = 18.85 \text{ rad/m}$$

$$\text{Phase velocity } u \text{ or } v_p = \frac{\omega}{\beta} = \frac{2\pi \times 600 \times 10^6}{18.85}$$

$$= 2 \times 10^8 \text{ m/s}$$

(P3)

- 3) A distortionless transmission line operating at 250 MHz has $R = 30 \Omega/m$, $L = 200 \mu H/m$ and $C = 80 pF/m$.

(a) Determine the characteristic Impedance Z_0 , the propagation constant γ and the velocity of propagation along the line.

(b) After how many meters travelling along the line will the voltage wave get reduced to 30% of its initial value?

(c) How far should the voltage wave travel along the line in order to undergo a phase shift of 20° .

Solution: @ For a distortionless line $\frac{R}{L} = \frac{G}{C}$

$$Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{200 \times 10^{-9}}{80 \times 10^{-12}}} = 50 \Omega$$

propagation constant γ given by

$$\gamma = \alpha + j\beta = \sqrt{(R+jWL)(G+jWC)}$$

$$\text{But } \frac{R}{L} = \frac{G}{C} \Rightarrow G = \frac{R}{L} C$$

$$\gamma = \alpha + j\beta = \sqrt{(R+jWL)(\frac{R}{L}C + jWC)}$$

$$\gamma = \alpha + j\beta = \sqrt{(R+jWL)(\frac{C}{L})(R + jWL)}$$

$$\gamma = \alpha + j\beta = (R+jWL) \sqrt{\frac{C}{L}}$$

$$\gamma = \alpha + j\beta = R \sqrt{\frac{C}{L}} + j\omega \sqrt{LC}$$

$$\gamma = 30 \sqrt{\frac{80 \times 10^{-12}}{200 \times 10^{-9}}} + j 2\pi \times 250 \times 10^6 \sqrt{200 \times 10^{-9} \times 80 \times 10^{-12}}$$

$$\gamma = 0.6 + j 6.2832 / m$$

$$\gamma = 0.6 + j 6.2832 \text{ /m}$$

(P4)

$$\gamma = 0.6 + j 6.2832 \text{ /m}$$

$$\gamma = \alpha + j \beta$$


Attenuation constant $\alpha = 0.6 \text{ Np/m}$ ($\beta = \text{phase constant} = 6.2832 \text{ rad/m}$)

The velocity of propagation or phase velocity is given by

$$u \text{ or } v_p = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{200 \times 10^{-9} \times 80 \times 10^{-12}}} \text{ m/s}$$

$$= 2.5 \times 10^8 \text{ m/s}$$

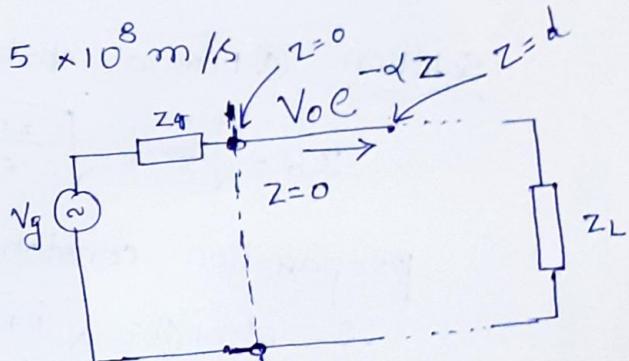

(b)

Let us assume that the wave is travelling along +ve z-direction and the magnitude of voltage wave be V_0 at $z=0$. The magnitude of this voltage wave at any arbitrary position along the line would then given by $V_0 e^{-\alpha z}$. The reflected wave is not considered.

Assume at $z=d$, the magnitude of this wave get reduced to 30% of V_0 .

$$V_0 e^{-\alpha d} = 0.3 V_0$$

$$\Rightarrow e^{-\alpha d} = 0.3$$

$$\ln e^{-\alpha d} = \ln 0.3$$

(P5)

$$-\alpha d = -1.2039$$

$$d = \frac{1.2039}{\alpha} = \frac{1.2039}{0.6} = 2.006 \text{ m}$$

(c) As the wave travels along the line, it would continuously undergo a phase shift. If it is assumed that the wave is travelling along the +z direction and at the initial position this wave is expressed as $V_0 e^{-j\phi_0}$, then this wave can be expressed at any arbitrary position along the line by $V_0 e^{-j\beta z}$.

$$\text{At } z=l \quad \beta l = 20^\circ \times \frac{\pi}{180} \text{ radians}$$

i.e After travelling 'l' m phase shift will be 20° or $\frac{20 \times \pi}{180}$ radians

$$\beta l = 20 \times \frac{\pi}{180}$$

$$6.2832 l = 20 \times \frac{\pi}{180}$$

$$l = \frac{20 \times \frac{\pi}{180}}{6.2832} = 5.56 \times 10^{-2} \text{ m}$$
$$= 55.56 \times 10^3 \text{ m}$$

(P6)

- 4) A 50Ω lossless transmission line is terminated by a load impedance $Z_L = 50 - j75\Omega$. If the incident power is 100mW , find the power delivered by the load.

Solution: Reflection coefficient $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$

$$= \frac{(50 - j75) - (50)}{(50 - j75) + 50}$$

$$= 0.36 - j0.48$$

$$= 0.6 e^{-j0.93}$$

$$P_t = (1 - |\Gamma|^2) P_i$$

$$P_t = (1 - |0.6|^2) \times 100 \times 10^{-3}$$

$$P_t = 64 \text{ mW}$$

(PF)

- 5) A transmission line operating at 500 M rad/sec
 has $L = 0.5 \mu\text{H/m}$, $C = 32 \text{ pF/m}$, $G = 100 \mu\text{V/m}$
 and $R = 25 \Omega/\text{m}$

- (a) calculate values of γ , α , β , u , λ and z_0
 (b) what distance down the line can a voltage
 wave travel before it is reduced to 10% of
 its initial value of amplitude?
 (c) what distance must it travel to undergo a
 90° phase shift?

Solution: $\text{① } L = 0.5 \mu\text{H/m} \quad C = 32 \text{ pF/m}, \quad G = 100 \mu\text{V/m}$

$$R = 25 \Omega/\text{m}$$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$\gamma = \sqrt{(25 + j \cancel{500 \times 10^6 \times 0.5 \times 10^{-6}})(100 \times 10^{-6} + j \frac{\cancel{500 \times 10^6}}{32 \times 10^{-12}})}$$

$$\gamma = 0.1061 + j 2.002/\text{m}$$

$$\gamma = \alpha + j\beta$$

$$\alpha = 0.1061 \quad \beta = 2.002$$

Wave length $\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{2.002} = 3.14 \text{ m}$

Phase velocity

$$u \text{ or } v_p = \frac{\omega}{\beta} = \frac{500 \times 10^6}{2.002} \\ = 2.5 \times 10^8 \text{ m/s}$$

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{25 + j 500 \times 10^6 \times 0.5 \times 10^{-6}}{100 \times 10^{-6} + j 500 \times 10^6 \times 32 \times 10^{-12}}} \\ = 125.3 \angle -2.68^\circ \Omega$$