



DVLSI PROJECT

18.04.2022

Jacob V Sanoj

ECE

Sem 4

B Section

PES1UG20EC083


TOPIC : D FLIP FLOP

Overview


The D flip-flop is a clocked flip-flop with a single digital input 'D'. Each time a D flip-flop is clocked, its output follows the state of 'D'. The D Flip Flop has only two inputs D and Clock Pulse. The D inputs go precisely to the S input and its complement is used to the R input.

It is a rising edge flip-flop which means that the output is decided when the clock reached 50% of its final value.

Schematic

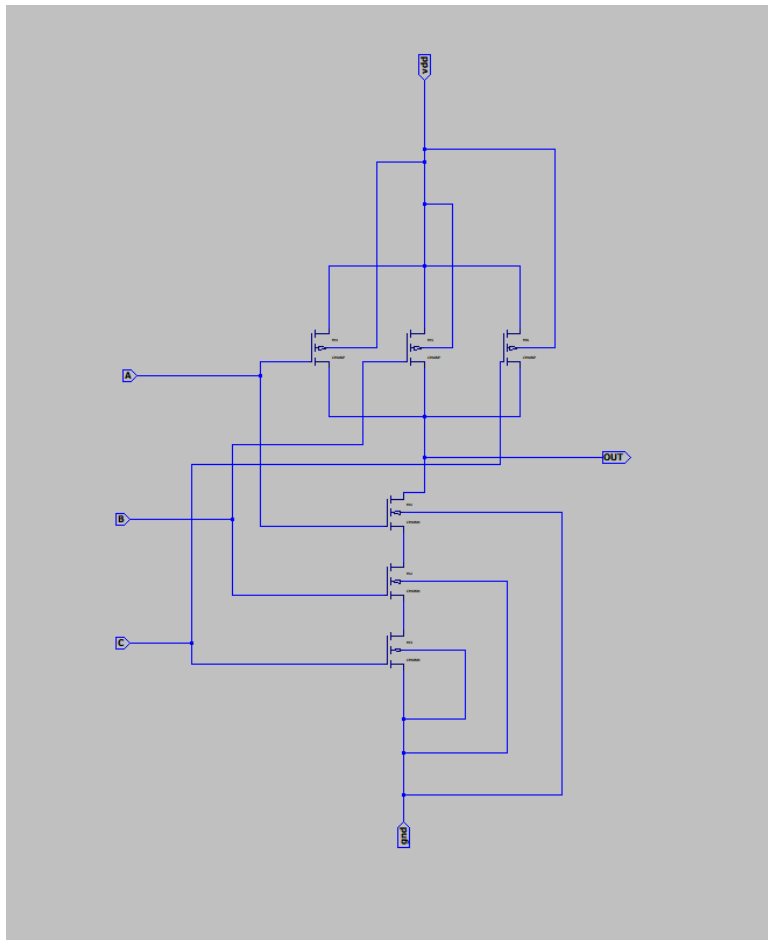


Symbol

 


Specifications

- I. Number of CMOS Used is 6
- II. Length of the CMOS 180 nm
- III. Width of the CMOS 2 μm

Testbench

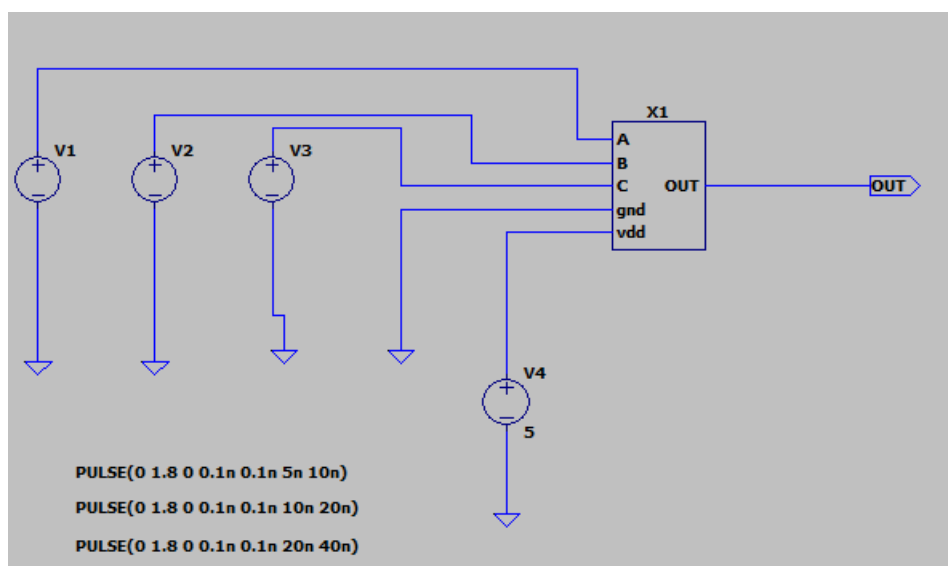

 

Observations


For $A = B = C = 1$, the output of the NAND Gate is 0 V

Power Dissipated is 467.93 μW


Delay is 2.14 ns

D Flip-Flop

Schematic

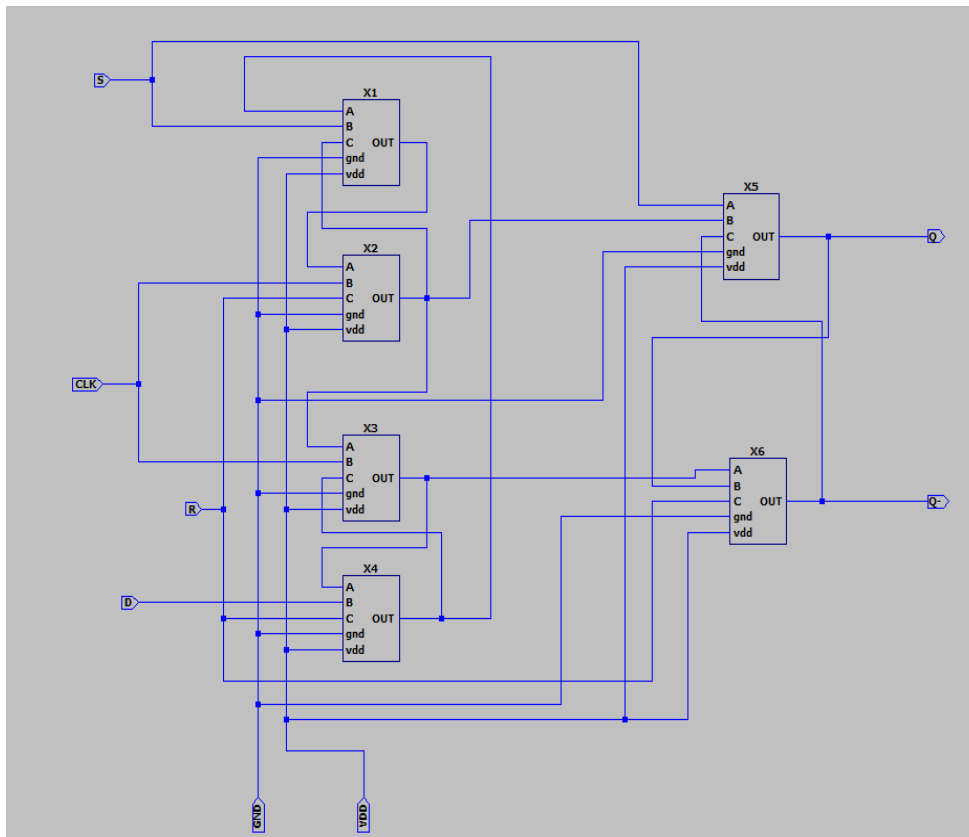

Symbol

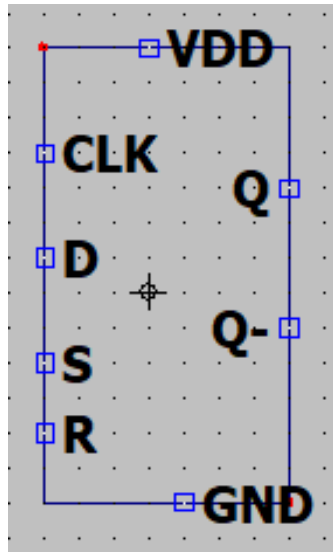

Specifications


Number of CMOS Used is 36

Length of the CMOS 180 nm

Width of the CMOS 2 μm

Test Parameters


- I. When $S=1$ and $R=1$

 

Power Dissipation = -332.05 μ W

II. When $S=0$ and $R=1$

Expected Output $Q=1$ AND $Q'=0$

 


$Q=4.889\text{ V}$ AND $Q'=2\text{ mV}$

Power Dissipation = $209.35\text{ }\mu\text{W}$

III. When $S=1$ and $R=0$

Expected Output $Q=0$ AND $Q'=1$

 

Power Dissipation = 86.03 μ W

Results

We have successfully a designed and implement D Flip-Flop using CMOS Structure