

Unit-5

(1)

TRANSMISSION LINES

Electromagnetic waves can propagate through

- (i) Unbounded media
Eg. TV broadcasting

- (ii) Guided structures

Eg: Transmission lines, waveguides

In this unit we will consider wave propagation through transmission lines. Transmission lines can be analyzed using

(i) EM Field theory

(ii) Electric circuit theory

Transmission lines analyzed from Electro-

- Magnetic field theory is complex, because it involves variables (x, y, z, t). Therefore it is not preferred.


Transmission lines analyzed from Electric

Circuit theory involves transmission line parameters R = Resistance per unit length, L = Inductance per unit length and C = Capacitance per unit length. It is simple and convenient for analysis.


G = Conductance per unit length

Different types of transmission lines


(2)

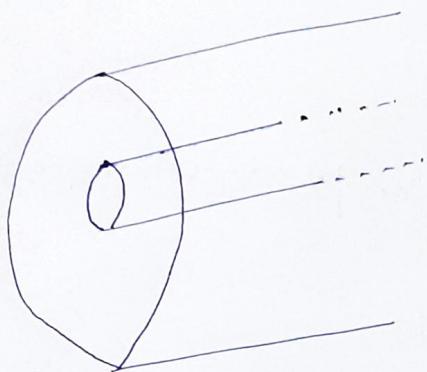

COAXIAL LINE

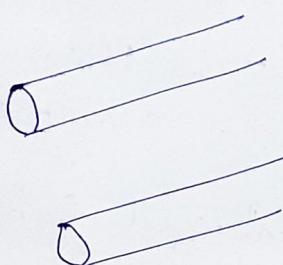

TWO WIRE LINE

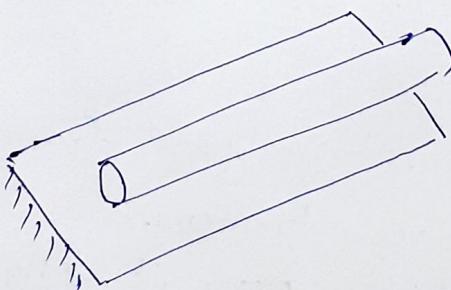





WIRE ABOVE CONDUCTING PLANE

Two types of transmission lines
Coaxial line has signal in the inner part

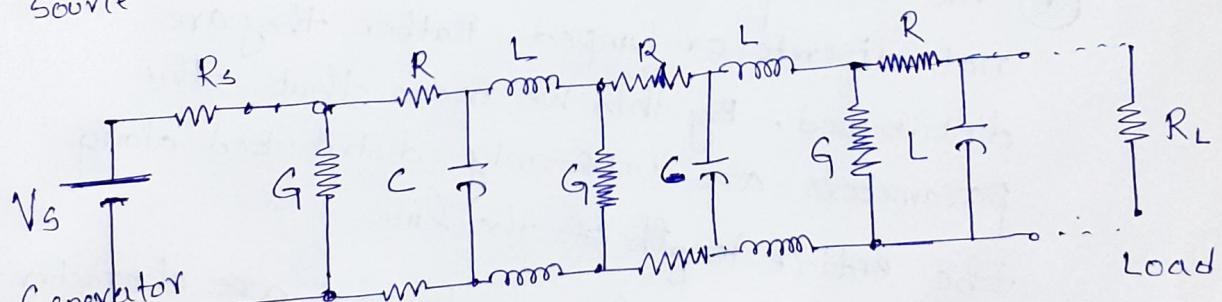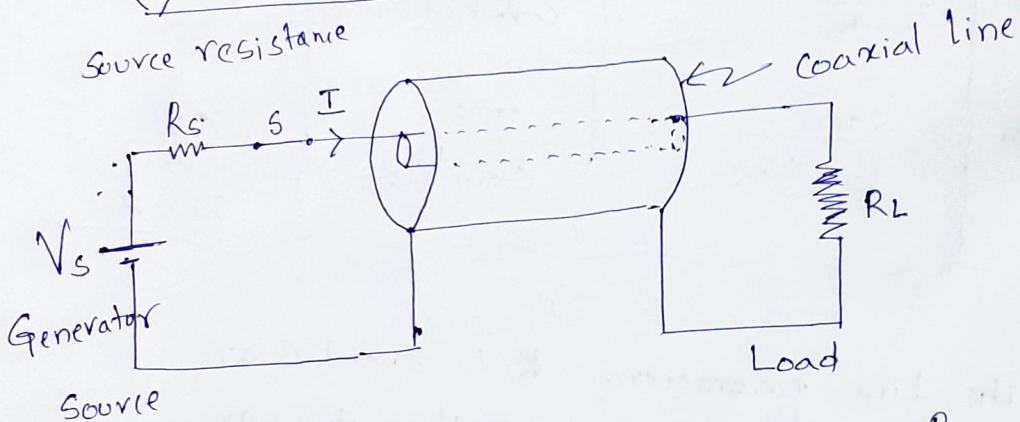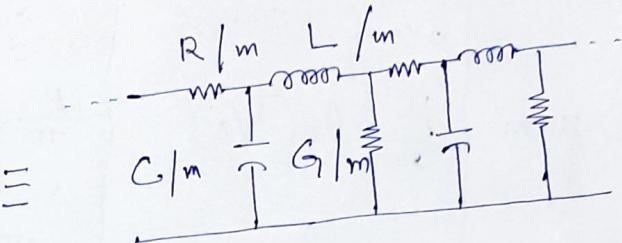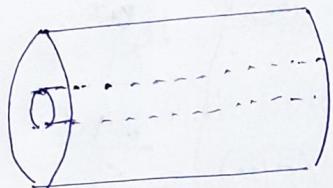(3)

TRANSMISSION LINE PARAMETERS

Consider a coaxial cable which is a transmission line. This can be represented by distributed parameters as follows



Source

Generalized
Distributed Parameters of a two conductor
transmission Line

4

Distributed Line Parameters at High Frequencies

Parameter	Coaxial line	Two-wire line	Planar line
$R \Omega/m$	$\frac{1}{2\pi\delta\omega_c} \left[\frac{1}{a} + \frac{1}{b} \right]$ $\delta \ll a, b$	$\frac{1}{\pi a \delta\omega_c}$ $\delta \ll a$	$\frac{2}{W\delta\omega_c}$ $\delta \ll t$
$L H/m$	$\frac{\mu}{2\pi} \ln(b/a)$	$\frac{\mu}{\pi} \cosh^{-1}(d/2a)$	$\frac{\mu d}{W}$
$G S/m$	$\frac{2\pi\omega}{b}$	$\frac{\pi\omega}{\cosh^{-1}(d/2a)}$	$\frac{\omega W}{d}$
$C F/m$	$\frac{2\pi\epsilon}{\ln(b/a)}$	$\frac{\pi\epsilon}{\cosh^{-1}(d/2a)}$	$\frac{\epsilon W}{d}$ $W \gg d$

① The line parameters R, L, G and C are not discrete or lumped. Rather, they are distributed. By this we mean that the parameters are uniformly distributed along the entire length of the line.

② For each line, the conductors are characterized by $\omega_c, \mu_c, \epsilon_c = \epsilon_0 \epsilon_r$ and the homogeneous dielectric separating the conductors is characterized by ω, μ, ϵ




(5)

3) $G \neq \frac{1}{R}$. R is the ac resistance per unit length of the conductors comprising the line, and G is the conductance per unit length due to the dielectric medium separating the conductors.

4) ' L ' is the external inductance per unit length, that is $L = L_{ext}$. The effects of internal inductance L_{in} ($= R/\omega$) are negligible at the high frequencies at which most communication system operate


5) For each line,
 $L_C = \mu \epsilon$ and $\frac{G}{C} = \frac{\omega}{\epsilon}$

(6)

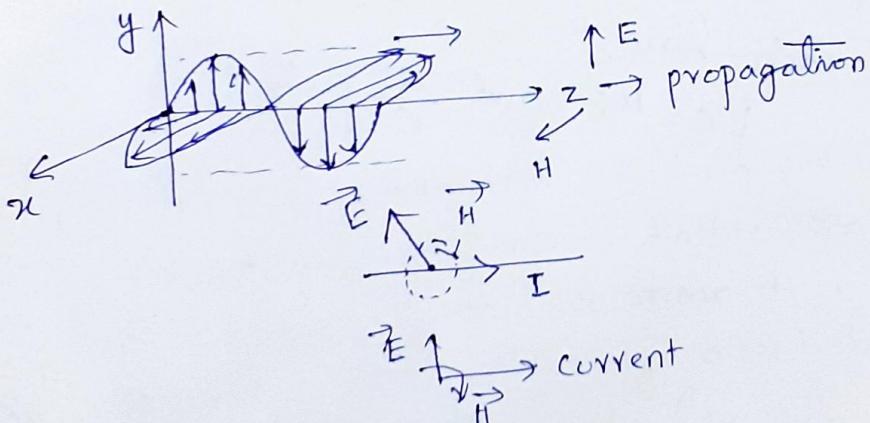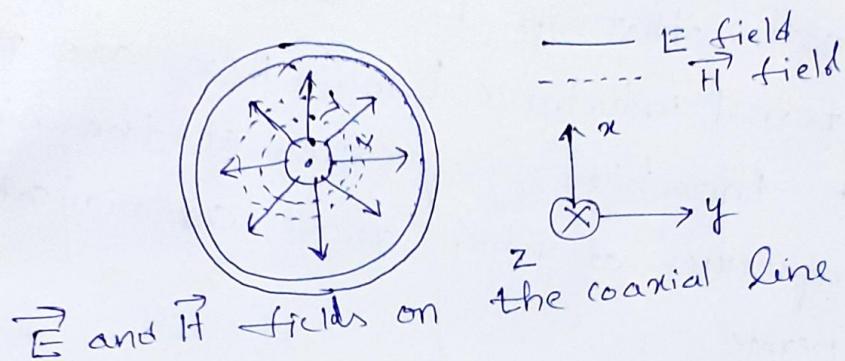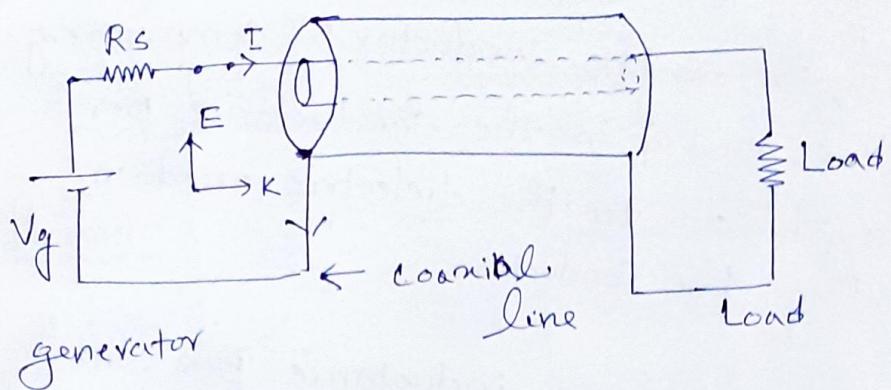

(f)

TRANSMISSION LINE EQUATIONS

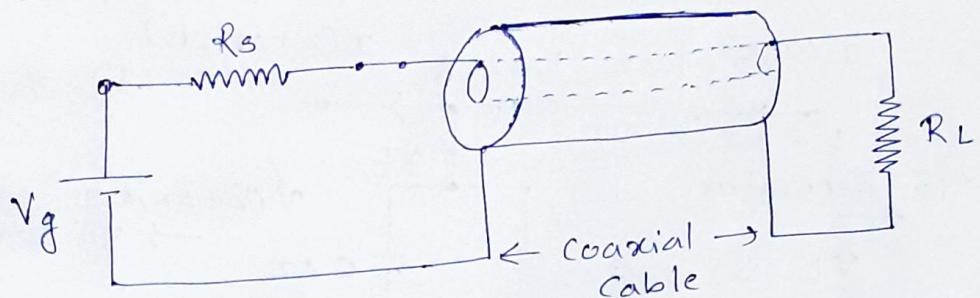

A two conductor transmission line supports a TEM wave, that is, the electric and magnetic fields on the line are perpendicular to each other and transverse to the direction of wave propagation.

An important property of TEM wave, waves is that the fields \vec{E} and \vec{H} are uniquely related to voltage "V" and current "I" respectively

$$V = - \int_{L}^{\infty} \vec{E} \cdot d\vec{l} \quad \text{hand formula}$$

$$I = \oint \vec{H} \cdot d\vec{l}$$


In view of this, we will use circuit quantities V and I in solving the transmission line.

with, balanced
ratios etc.

$$\left[\frac{V + (f_s \cdot sA + s) V_{SAP}}{[(f_s \cdot sA) V] \frac{G}{sA} + sA} \right] + (f_s \cdot sA + s) I = (f_s \cdot s) I$$

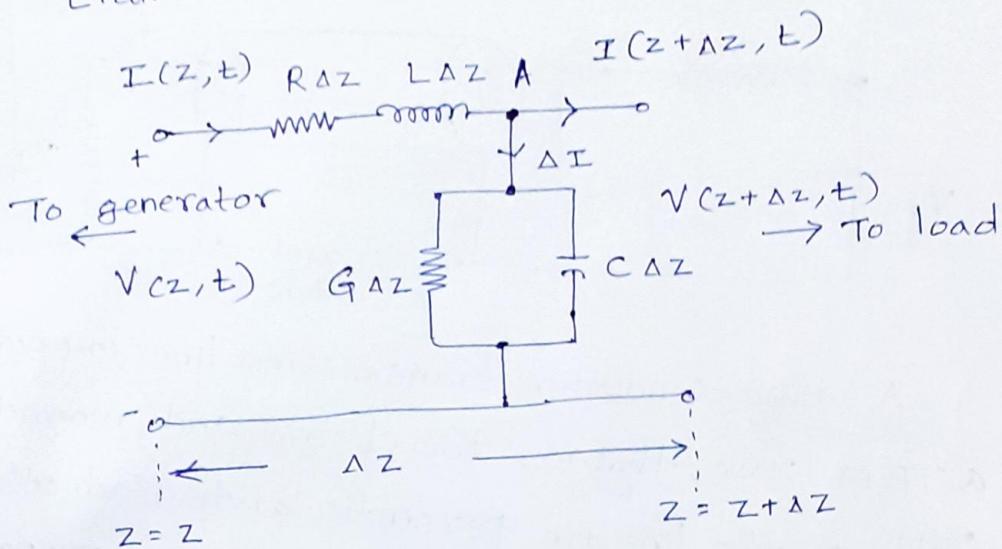(8)

The equivalent circuit of a portion of the transmission line can be represented as



This type of equivalent circuit model is called an L-type equivalent circuit model.

By applying Kirchoff's Voltage Law to the outer loop of the circuit we get

$$V(z, t) - R\Delta z I(z, t) - L\Delta z \frac{dI(z, t)}{dt} - V(z + \Delta z, t) = 0$$

$$-\frac{[V(z + \Delta z, t) - V(z, t)]}{\Delta z} = RI(z, t) + L \frac{dI(z, t)}{dt}$$

Taking the limit $\Delta z \rightarrow 0$

$$-\frac{dV(z, t)}{dz} = RI(z, t) + L \frac{dI(z, t)}{dt} \rightarrow (1)$$

Applying KCL at node A

$$I(z, t) = I(z + \Delta z, t) + \Delta I$$

$$I(z, t) = I(z + \Delta z, t) + \left[G\Delta z V(z + \Delta z, t) + C\Delta z \frac{d(V(z + \Delta z, t))}{dt} \right]$$

$i_c = C \frac{dV}{dt}$
current through the capacitor

(9)

$$-\frac{[I(z+\Delta z, t) - I(z, t)]}{\Delta z} = G V(z+\Delta z, t) + C \frac{dV(z+\Delta z, t)}{dt}$$

As $\Delta z \rightarrow 0$

$$-\frac{dI(z, t)}{dz} = G V(z, t) + C \frac{dV(z, t)}{dt} \rightarrow (2)$$

If we assume harmonic time dependence $\propto e^{j\omega t}$

$$\text{that } V(z, t) = \Re [V_s(z) e^{j\omega t}] \rightarrow (3)$$

$$I(z, t) = \Re [I_s(z) e^{j\omega t}] \rightarrow (4)$$

In equation (3) and (4) $V_s(z)$ and $I_s(z)$ are the phasor forms of $V(z, t)$ and $I(z, t)$

From (1) we have

$$-\frac{dV(z, t)}{dz} = R I(z, t) + L \frac{dI(z, t)}{dt}$$

$$-\frac{d}{dz} [\Re [V_s(z) e^{j\omega t}]] = R \cdot \Re [I_s(z) e^{j\omega t}]$$

$$+ L \frac{d}{dt} [\Re [I_s(z) e^{j\omega t}]]$$

$$-\Re \left[\frac{dV_s(z)}{dz} e^{j\omega t} \right] = R \cdot \Re [I_s(z) e^{j\omega t}]$$

$$+ L [\Re I_s(z) j\omega e^{j\omega t}]$$

cancelling $\Re \{ \}$ and $e^{j\omega t}$ on both sides

$$-\frac{dV_s}{dz} = R I_s + j\omega L I_s = (R + j\omega L) I_s \rightarrow (5)$$

(10)

From (2)

$$-\frac{d}{dz} I(z, z) = G V(z, z) + C \frac{dV}{dt}(z, z)$$

$$-\frac{d}{dz} \operatorname{Re}[I_s(z) e^{j\omega t}] = G \operatorname{Re}[V_s(z) e^{j\omega t}] + C \frac{d}{dt} [\operatorname{Re}[V_s(z) e^{j\omega t}]]$$

$$-\operatorname{Re}\left[\frac{dI_s(z)}{dz} e^{j\omega t}\right] = \operatorname{Re}[GV_s(z) e^{j\omega t}] + \operatorname{Re}[j\omega C V_s(z) e^{j\omega t}]$$

Cancelling $\operatorname{Re}\{ \}$ and $e^{j\omega t}$ on both sides

$$-\frac{dI_s(z)}{dz} = (G + j\omega C) V_s(z)$$

$$-\frac{dI_s}{dz} = (G + j\omega C) V_s \rightarrow (6)$$

$$\text{Consider } -\frac{dV_s}{dz} = (R + j\omega L) I_s$$

differentiating on both sides w.r.t. z

$$-\frac{d^2V_s}{dz^2} = (R + j\omega L) \frac{dI_s}{dz} \rightarrow (7)$$

$$-\frac{d^2V_s}{dz^2} = (R + j\omega L) (- (G + j\omega C)) V_s$$

$$-\frac{d^2V_s}{dz^2} = -(R + j\omega L)(G + j\omega C) V_s$$

$$+\frac{d^2V_s}{dz^2} = +j^2 V_s$$

~~$\frac{d^2V_s}{dz^2} = j^2 V_s$~~

$$\frac{d^2V_s}{dz^2} - j^2 V_s = 0$$

(8)

11

Where $\gamma = \alpha + j\beta$

$$\gamma = \sqrt{(R+jWL)(G+jWC)}$$

→ (9)

Where α = Attenuation constant in Np/m or decibel/m β = Phase constant in radians/meter γ = Propagation constant

$$\lambda = \frac{2\pi}{\beta} \rightarrow (10)$$

Multiply f on both sides

$$\lambda f = \frac{2\pi f}{\beta}$$

$$v = \frac{\omega}{\beta} = f\lambda = \text{Velocity} \rightarrow (11)$$

Consider $\frac{d^2V_s}{dz^2} - v^2 V_s = 0 \rightarrow (12)$

The solution to equation (12) is given by

$$V_s(z) = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z} \rightarrow (13)$$

Where ~~V_{s0}~~ V_o^+ , V_o^- , I_o^+ and I_o^- arewave amplitudes, travelling in $+z$ -direction $e^{-\gamma z}$ denote the wave travelling in $+z$ -direction → $e^{+\gamma z}$ denote the wave travelling in $-z$ -direction ←

$$V(z, t) = \operatorname{Re} [V_s(z) e^{j\omega t}]$$

(12)

$$= \operatorname{Re} [V_o e^{\pm j\beta z}]$$

$$= \operatorname{Re} [V_o^+ e^{-\gamma z} e^{j\omega t} + V_o^- e^{+\gamma z} e^{j\omega t}]$$

$$= \operatorname{Re} [V_o^+ e^{-\gamma z} \cdot e^{-j\beta z} \cdot e^{j\omega t} + V_o^- e^{+\gamma z} \cdot e^{+j\beta z} e^{j\omega t}]$$

$$= V_o^+ e^{-\gamma z} \cos(\omega t - \beta z) + V_o^- e^{\gamma z} \cos(\omega t + \beta z)$$

$$\text{Hence } I_s(z) = I_o^+ e^{-\gamma z} + I_o^- e^{+\gamma z}$$

Characteristic Impedance "Z_o"

The characteristic impedance "Z_o" of the line is

the ratio of the positively travelling voltage wave to the current at any point on the line.

$$\text{Consider } V = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z}$$

$$I_s = I_o^+ e^{-\gamma z} + I_o^- e^{+\gamma z}$$

$$\text{consider } V = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z}$$

differentiating with respect z

$$\frac{dV}{dz} = (-\gamma) V_o^+ e^{-\gamma z} + (\gamma) V_o^- e^{+\gamma z} \rightarrow (1)$$

$$\text{But } \frac{dV}{dz} = -(R+j\omega L) I_s$$

$$\frac{dV}{dz} = -(R+j\omega L)(I_o^+ e^{-\gamma z} + I_o^- e^{+\gamma z}) \rightarrow (2)$$

(13)

$$\textcircled{1} = \textcircled{2}$$

$$-(R+j\omega L) I_o^+ e^{-jz} - (R+j\omega L) I_o^- e^{+jz} = -V_o^+ e^{-jz} + V_o^- e^{+jz}$$

(2)

Equaling the coefficients e^{-jz} on both sides

$$\therefore (R+j\omega L) I_o^+ = V_o^+$$

$$\frac{V_o^+}{I_o^+} = \frac{(R+j\omega L)}{\downarrow}$$

$$\frac{V_o^+}{I_o^+} = \frac{(R+j\omega L)}{\sqrt{(R+j\omega L)(G+j\omega C)}}$$

$$\boxed{\frac{V_o^+}{Z_o^+} = Z_o = \sqrt{\frac{R+j\omega L}{G+j\omega C}}} = R_o + jX_o$$

Similarly if we equate the coefficients of e^{+jz}
we get
 $-(R+j\omega L) I_o^- = V_o^-$
 $\frac{V_o^-}{I_o^-} = \frac{(R+j\omega L)}{\downarrow}$

$$\frac{V_o^-}{I_o^-} = Z_o = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

R_o is the real part of Z_o
 X_o is the imaginary part of Z_o

$$\therefore Z_o = \frac{1}{Y_o} \quad Y_o = \text{characteristic Admittance}$$

There are three types of transmission line
they are (i) Lossless Transmission Line
(ii) Distortionless Transmission Line
(iii) General transmission line

1) Lossless Line ($R=0, G=0$)

(14)

A transmission line is said to be lossless, if the conductors of the line are perfect conductors i.e. $\alpha_c = \infty$ and the dielectric medium separating them is lossless, i.e. whose conductivity $\alpha = 0$

\therefore Since $\alpha_c = \infty, \alpha = 0$

$$R = 0$$

$$G = 0$$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$\gamma = \sqrt{(0+j\omega L)(0+j\omega C)}$$

$$\gamma = j\omega \sqrt{LC}$$

$$\gamma = \alpha + j\beta$$

$$\therefore \alpha = 0 \quad \beta = \omega \sqrt{LC}$$

$$\text{Velocity } u = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

$$u = f\lambda$$

$$Z_0 = \sqrt{\left(\frac{R + j\omega L}{G + j\omega C} \right)}$$

$$Z_0 = R_0 = \sqrt{\frac{L}{C}} \quad (\text{iii})$$

2) Distortionless Line ($\frac{R}{L} = \frac{G}{C}$) (15)

A signal normally consists of a band of frequencies, wave amplitudes of different frequency components will be attenuated differently in a lossy line because ' α ' is frequency dependent. Since, in general, the phase velocity of each frequency component is also frequency dependent, this will result in distortion.

A distortionless line is one in which the attenuation constant ' α ' is frequency independent while the phase constant ' β ' is linearly dependent on frequency.

For a distortionless line

$$\frac{R}{L} = \frac{G}{C} \rightarrow (1)$$

We know $\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$

$$\gamma = \sqrt{RG \left(1 + j\omega \frac{L}{R}\right) \left(1 + j\omega \frac{C}{G}\right)} \rightarrow (2)$$

$$\gamma = \sqrt{RG} \left(1 + j\omega \times \frac{C}{G}\right)^{1/2} \left(1 + j\omega \frac{C}{G}\right)^{1/2} \text{ using (1) in (2)}$$

$$\gamma = \sqrt{RG} \left(1 + j\omega \frac{C}{G}\right) = \alpha + j\beta \rightarrow (3)$$

$$\therefore \alpha = \sqrt{RG} \quad (\beta = \omega \sqrt{RG} \frac{C}{G} = \frac{\omega \sqrt{R}}{\sqrt{G}} \times C)$$

$$\beta = \omega \sqrt{\frac{L}{C}} \times C = \omega \sqrt{LC}$$

Since $\alpha = \sqrt{RG}$ does not depend on frequency,
where as ' β ' is a linear function of frequency, because

$$\beta = \omega \tan$$

(16)

$$Z_0 = \sqrt{\frac{(R + j\omega L)}{(G + j\omega C)}}$$

$$Z_0 = \sqrt{\frac{R(1 + j\omega L/R)}{G(1 + j\omega C/G)}}$$

$$Z_0 = \sqrt{\frac{R}{G}} \times \frac{(1 + j\omega L/k)}{(1 + j\omega C/k)}$$

$$Z_0 = \sqrt{\frac{R}{G}} = \sqrt{\frac{L}{C}} = R_0 + jX_0$$

$$\therefore R_0 = \sqrt{\frac{R}{G}} = \sqrt{\frac{L}{C}}, X_0 = 0$$

$$\text{velocity } u = \frac{\omega}{\beta} = \frac{\omega}{\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}} = f\lambda$$

The phase velocity is independent of
frequency because the phase constant β
linearly depends on frequency.

Transmission Line Characteristics

(17)

Care

Propagation Constant

$$\gamma = \alpha + j\beta$$

Characteristic Impedance

$$Z_0 = R_0 + jX_0$$

General

$$\sqrt{(R+j\omega L)(G+j\omega C)}$$

$$\sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

Lossless

$$0 + j\omega\sqrt{LC}$$

$$\sqrt{\frac{L}{C}} + j0$$

Distortionless
line

$$\sqrt{RG} + j\omega\sqrt{LC}$$

$$\sqrt{\frac{L}{C}} + j0$$

- *) A lossless line is also distortionless, but a distortionless is not necessarily lossless
- *) Lossless lines are desirable in power transmission
- *) Telephone lines are required to be ~~lossless~~ distortionless.

Problems

(18)

- 1) An air line has a characteristic impedance of 70Ω and a phase constant of 3 rad/m at 100 MHz . Calculate the inductance per meter and the capacitance per meter of the line.

Solution

An air line can be regarded as a lossless line because $\alpha = 0$ and $\alpha_c = b$

For a lossless line $R=0$, $G=0$

$$\therefore \alpha = 0$$

$$Z_0 = R_0 = \sqrt{\frac{L}{C}}$$

$$\beta = \omega \sqrt{LC}$$

$$\frac{(Z_0 = R_0)}{\beta} = \frac{1}{\omega C}$$

$$C = \frac{\beta}{(\omega R_0)^2} = \frac{3}{2 \times \pi \times 100 \times 10^6 \times 70} \rightarrow Z_0$$

where $R_0 = Z_0$

$$C = 68.2 \times 10^{-12} \text{ F/m}$$

$$L = R_0^2 C = (70)^2 (68.2 \times 10^{-12})$$

$$L = 334.2 \times 10^{-9} \text{ H/m}$$

(19)

- 2) A distortionless line has $Z_0 = 60 \Omega$, $\alpha = 20 \text{ m}^{-1}/\text{m}$, $u = 0.6c$, where c is the speed of light in Vacuum. Find R , L , G , C and λ at 100 MHz.

Solution:

For a distortionless line

$$RC = GL$$

$$G = \frac{RC}{L}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$\alpha = \sqrt{RG} = R \sqrt{\frac{C}{L}} = \frac{R}{Z_0}$$

$$R = \alpha Z_0$$

$$u = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

$$R = \alpha Z_0 = (20 \times 10^3) 60 = 1.2 \times 10^2 \Omega/\text{m}$$

$$u = \frac{1}{\sqrt{LC}} \Rightarrow u^2 = \frac{1}{LC} \quad L = \frac{1}{u^2 C}$$

$$L = \frac{1}{u^2 C} \times \frac{Z_0}{Z_0}$$

$$L = \frac{Z_0}{\frac{1}{u^2 C} \times \alpha \times \sqrt{\frac{L}{C}}} = \frac{Z_0}{\frac{1}{\sqrt{LC}}} = \frac{Z_0}{u}$$

$$L = \frac{Z_0}{u} = 333 \times 10^{-9} \text{ H/m}$$

(20)

$$G = \frac{\omega^2}{R} = \frac{400 \times 10^6}{1.2} = 333 \times 10^6 \text{ N/m}$$

$$uZ_0 = \frac{1}{c}$$

$$C = \frac{1}{uZ_0} = \frac{1}{0.6 \times 3 \times 10^8 \times 60}$$


$$C = 92.59 \times 10^{-12} \text{ F/m}$$

$$\lambda = \frac{u}{f} = \frac{0.6 \times 3 \times 10^8}{10^8} = 1.8 \text{ m}$$


(21)

Input Impedance, Standing Wave Ratio, And Power

Input Impedance:

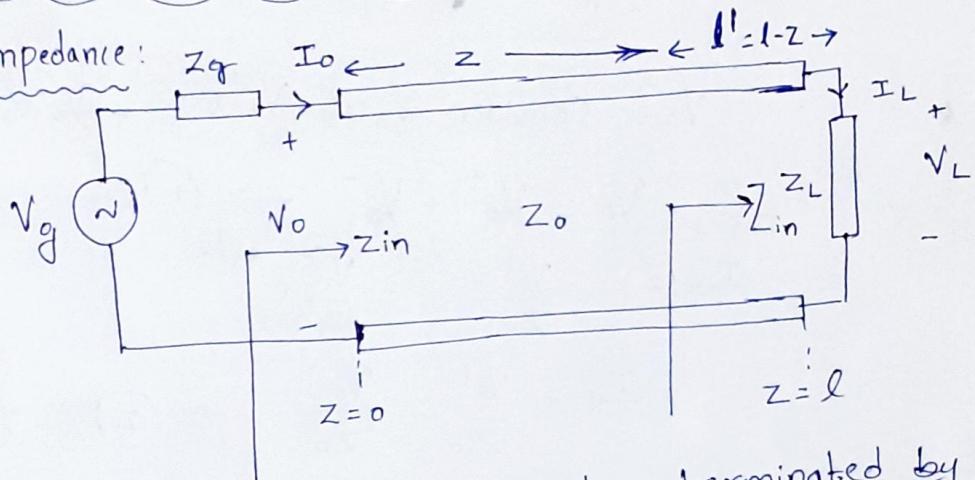

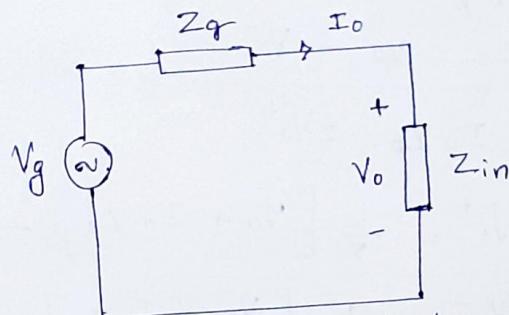Input Impedance due to a line terminated by a load.



Equivalent circuit for finding V_o and I_o in terms of Z_{in} at the input

Consider a transmission line of length " l ", characteristic impedance Z_0 , propagation constant " γ "

Let Voltage equation as a function 'z' is given by

$$V_s(z) = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z}$$

The current equation in terms of 'z' is given

$$I_s(z) = \frac{V_o^+}{Z_0} e^{-\gamma z} - \frac{V_o^-}{Z_0} e^{+\gamma z}$$

$$V_{s(z)} \Big|_{z=0} = V_o = V_o^+ + V_o^-$$

(22)

$$I_{s(z)} \Big|_{z=0} = I_o = I_o \frac{V_o^+}{Z_0} - \frac{V_o^-}{Z_0}$$

A. Consider $V_{s(z)} = V_o^+ e^{-jz} + V_o^- e^{+jz}$

$$V_o = V_o^+ + V_o^- \rightarrow (1)$$

$$I_{s(z)} = \frac{V_o^+}{Z_0} e^{-jz} - \frac{V_o^-}{Z_0} e^{+jz}$$

$$I_o = \frac{V_o^+}{Z_0} - \frac{V_o^-}{Z_0} \rightarrow (2)$$


$$V_o = V_o^+ + V_o^-$$

$$I_o Z_0 = V_o^+ - V_o^-$$

$$\underline{V_o + I_o Z_0 = 2V_o^+}$$

$$V_o^+ = \frac{1}{2} [V_o + I_o Z_0] \rightarrow (3)$$
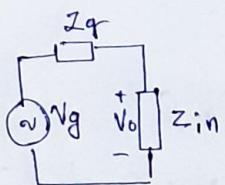
$$\text{Hence } V_o^- = \frac{1}{2} [V_o - I_o Z_0] \rightarrow (4)$$



$$V_o = \frac{Z_{in}}{Z_{in} + Z_g} V_g \quad I_o = \frac{V_g}{Z_{in} + Z_g}$$

on the other hand if we are given the conditions

$$V_L = V_{s(z)} \Big|_{z=l} \quad I_L = I_{s(z)} \Big|_{z=l}$$

$$V_L = V_o^+ e^{-jl} + V_o^- e^{+jl}$$

$$I_L = \frac{V_o^+}{Z_0} e^{-jl} - \frac{V_o^-}{Z_0} e^{+jl}$$

$$V_L = V_o^+ e^{-\gamma l} + V_o^- e^{+\gamma l} \rightarrow (5)$$

(23)

$$Z_0 I_L = V_o^+ e^{-\gamma l} - V_o^- e^{+\gamma l} \rightarrow (6)$$

$$(5) + (6) \quad V_L + Z_0 I_L = 2 V_o^+ e^{-\gamma l}$$

$$V_o^+ = \frac{1}{2} [V_L + Z_0 I_L] e^{+\gamma l} \rightarrow (7)$$

$$(5) - (6) \quad V_L - Z_0 I_L = 2 V_o^- e^{+\gamma l}$$

$$V_o^- = \frac{1}{2} [V_L - Z_0 I_L] e^{-\gamma l} \rightarrow (8)$$

$$Z_{in} = \left. \frac{V_s(z)}{I_s(z)} \right|_{z=0} = \frac{\cancel{V_o^+ e^{-\gamma l}} + \cancel{V_o^- e^{+\gamma l}}}{\frac{V_o^+ e^{-\gamma l}}{Z_0} - \frac{V_o^- e^{+\gamma l}}{Z_0}}$$

$$Z_{in} = \frac{Z_0 (V_o^+ + V_o^-)}{(V_o^+ - V_o^-)} \rightarrow (9) \rightarrow (9)$$

$$Z_{in} = \left. \frac{V_s(z)}{I_s(z)} \right|_{z=0} = \frac{\cancel{X_o^+ e^{-\gamma l}} + \cancel{X_o^- e^{+\gamma l}}}{\frac{\cancel{X_o^+ e^{-\gamma l}}}{Z_0} - \frac{\cancel{X_o^- e^{+\gamma l}}}{Z_0}}$$

$$= \frac{Z_0 [X_o^+ e^{-\gamma l} + X_o^- e^{+\gamma l}]}{[X_o^+ e^{-\gamma l} - X_o^- e^{+\gamma l}]}$$

using (7) and (8) ~~in (1)~~

$$\text{From (7)} \quad V_o^+ = \frac{1}{2} [V_L + z_0 I_L] e^{j\gamma l}$$

$$\text{From (8)} \quad V_o^- = \frac{1}{2} [V_L - z_0 I_L] e^{-j\gamma l}$$

$$\text{Since } V_L = I_L Z_L$$

$$(7) \text{ becomes } V_o^+ = \frac{1}{2} [I_L Z_L + z_0 I_L] e^{j\gamma l} \rightarrow (7a)$$

$$(8) \text{ becomes } V_o^- = \frac{1}{2} [I_L Z_L - z_0 I_L] e^{-j\gamma l} \rightarrow (8a)$$

using (7a) and (8a) in (1)

$$Z_{in} = z_0 \left[\frac{\frac{V_o^+}{V_o^+} + \frac{V_o^-}{V_o^-}}{\frac{V_o^+}{V_o^+} - \frac{V_o^-}{V_o^-}} \right]$$

$$Z_{in} = z_0 \left[\frac{\frac{1}{2} (I_L Z_L + I_L z_0) e^{j\gamma l} + \frac{1}{2} (I_L Z_L - I_L z_0) e^{-j\gamma l}}{\frac{1}{2} (I_L Z_L + I_L z_0) e^{j\gamma l} - \frac{1}{2} (I_L Z_L - I_L z_0) e^{-j\gamma l}} \right]$$

$$Z_{in} = z_0 \left[\frac{\frac{(z_L + z_0) e^{j\gamma l} + (z_L - z_0) e^{-j\gamma l}}{(z_L + z_0) e^{j\gamma l}}}{\frac{(z_L + z_0) e^{j\gamma l} - (z_L - z_0) e^{-j\gamma l}}{(z_L + z_0) e^{j\gamma l}}} \right]$$


$$Z_{in} = z_0 \left[\frac{z_L (e^{j\gamma l} + e^{-j\gamma l}) + z_0 (e^{j\gamma l} - e^{-j\gamma l})}{z_L (e^{j\gamma l} - e^{-j\gamma l}) + z_0 (e^{j\gamma l} + e^{-j\gamma l})} \right]$$

$$Z_{in} = z_0 \left[\frac{z_L + z_0 \tanh j\gamma l}{z_0 + z_L \tanh j\gamma l} \right]$$

$$\therefore \tanh j\gamma l = \frac{(e^{j\gamma l} + e^{-j\gamma l})/2}{(e^{j\gamma l} - e^{-j\gamma l})/2}$$

$Z_{in} = Z_0 \left[\frac{Z_L + Z_0 \tanh j\beta l}{Z_0 + Z_L \tanh j\beta l} \right]$ corresponds to lossy transmission line. It is a general expression for finding "Z_{in}" at any point on the line.

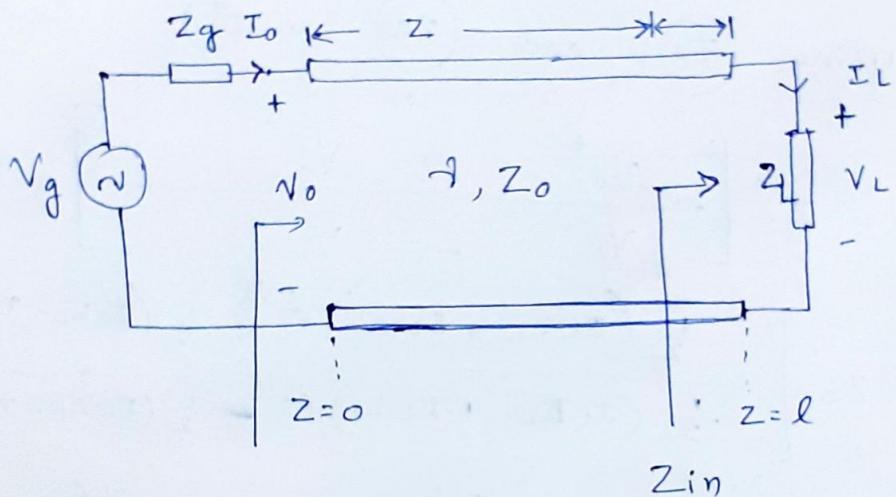To find "Z_{in}" at a distance "l'" from the load, we replace l by l'. where $l' = l - z$



For a lossless line $\alpha = 0$, $j = \alpha + j\beta = j\beta$
 $\tanh j\beta l = j \tan \beta l$ and $Z_0 = R_0$

$$\therefore Z_{in} = Z_0 \left[\frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} \right] \text{(lossless lines)}$$

" βl " is usually referred to as electrical length of the line and can be expressed in degrees or radians.

For a lossless line, the input impedance varies periodically with distance "l" from the load.

Reflection Coefficient or Voltage Reflection

Coefficient

Voltage Reflection coefficient Γ_L is the ratio of the reflected wave voltage to the incident wave voltage at the load.

$$\Gamma_L = \frac{\text{Voltage of the reflected wave}}{\text{Voltage of the incident wave}}$$

$$\Gamma_L = \frac{V_o^- e^{+j\ell}}{V_o^+ e^{-j\ell}}$$

But we know, at the load

$$V_o^- = \frac{1}{2} [I_L Z_L - I_L Z_0] e^{-j\ell}$$

$$V_o^+ = \frac{1}{2} [I_L Z_L + I_L Z_0] e^{+j\ell}$$

$$\Gamma_L = \frac{V_o^- e^{+j\ell}}{V_o^+ e^{-j\ell}} = \frac{\frac{1}{2} [I_L Z_L - I_L Z_0] e^{+j\ell} \cdot e^{-j\ell}}{\frac{1}{2} [I_L Z_L + I_L Z_0] e^{+j\ell} \cdot e^{-j\ell}}$$

$$\boxed{\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}}$$

The voltage reflection coefficient at any point on the line is the ratio of the reflected voltage to that of the incident wave

(27)

$$\text{In general } \Gamma(z) = \frac{V_o^- e^{jz}}{V_o^+ e^{-jz}} = \frac{V_o^-}{V_o^+} e^{2jz}$$

$$\text{If } z = l - l'$$

$$\Gamma(z) = \frac{V_o^-}{V_o^+} e^{2j(l-l')}$$

$$\Gamma(z) = \frac{V_o^-}{V_o^+} e^{2jl} e^{-2jl'}$$

$$\boxed{\Gamma(z) = \Gamma_L e^{-2jl'}}$$

The current reflection coefficient at any point on the line is the negative of the voltage reflection coefficient at that point.

$$\therefore \text{Current reflection Coefficient at the load} = \frac{I_o^- e^{jl}}{I_o^+ e^{-jl}} = -\Gamma_L$$

Standing Wave Ratio (s)

Standing Wave Ratio is denoted by "s"

$$s = \frac{V_{\max}}{V_{\min}} = \frac{I_{\max}}{I_{\min}} = \frac{|Z_{in}|_{\max}}{|Z_{in}|_{\min}} = \frac{1 + |Z_L|}{1 - |Z_L|}$$


$$I_{\max} = \frac{V_{\max}}{Z_0}$$

$$I_{\min} = \frac{V_{\min}}{Z_0}$$

$$|Z_{in}|_{\max} = \frac{V_{\max}}{I_{\min}} = s Z_0$$


$$|Z_{in}|_{\min} = \frac{V_{\min}}{I_{\max}} = \frac{Z_0}{s}$$

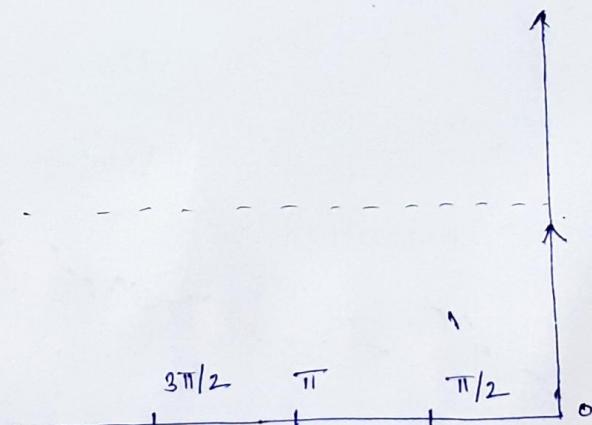Consider a lossless line with characteristic impedance of $Z_0 = 50\Omega$. For the sake of simplicity, we assume that the line is terminated in a pure resistive load $Z_L = 100\Omega$ and the voltage at the load is 100V (rms).



Voltage and current standing wave pattern on a lossless line terminated by a resistive load.

(29)

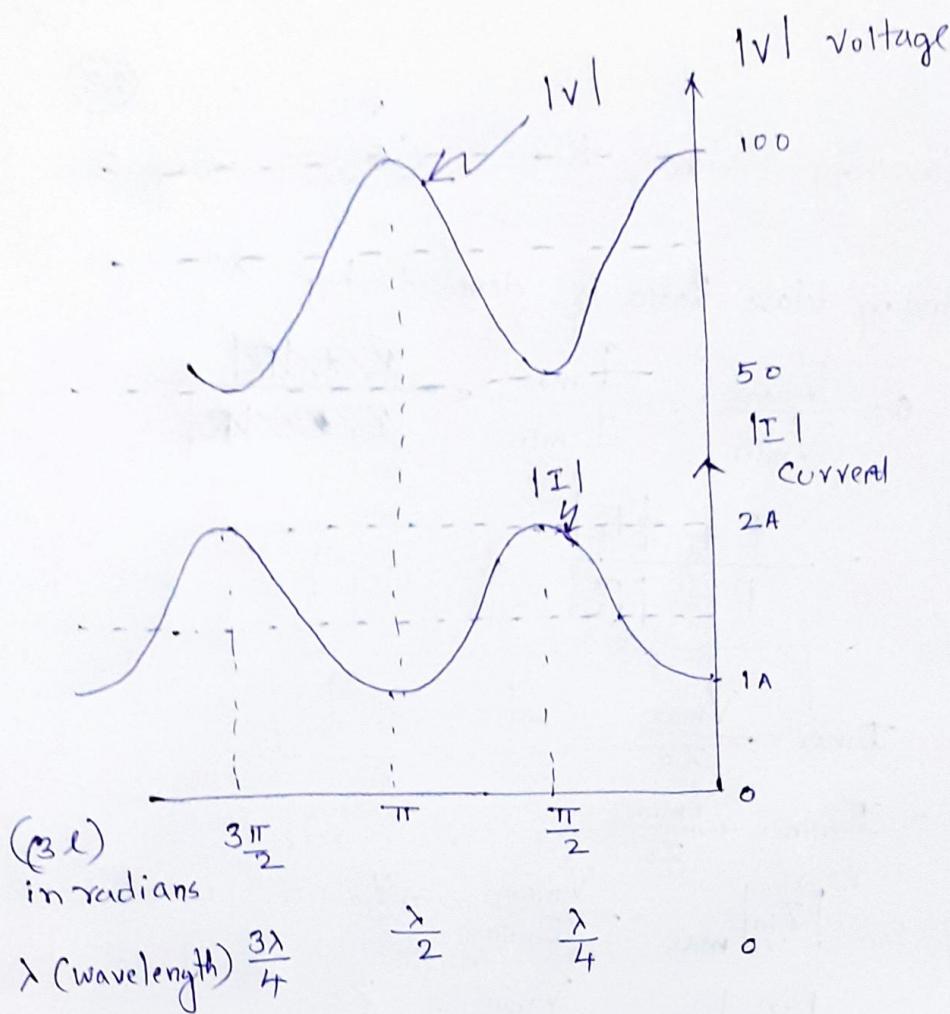

Voltage and current standing wave patterns on a lossless line terminated by a resistive load.

As we know from previous notes this option
will give us a full understanding with respect to