

# DVLSI PROJECT

NAME: Jacob V Sanoj

SRN: PES1UG20EC083

CLASS: 4 B

TOPIC: TRANSMISSION GATE

## Introduction:

A transmission gate (TG) is an analog gate similar to a relay that can conduct in both directions or block by a control signal with almost any voltage potential. It is a CMOS-based switch, in which PMOS passes a strong 1 but poor 0, and NMOS passes strong 0 but poor 1. Both PMOS and NMOS work simultaneously.


## Theory:

When the control input is a logic zero is given the gate of the n-channel MOSFET is also at a negative supply voltage potential. The gate terminal of the p-channel MOSFET is caused by the inverter, to the positive supply voltage potential. Regardless of which switching terminal of the transmission gate voltage is applied, the gate-source voltage of the n-channel MOSFETs is always negative, and the p-channel MOSFETs is always positive. Accordingly, neither of the two transistors will conduct and the transmission gate turns off.





Now using transmission gate, we are going to realise 2:1 MUX

Which has three inputs. A, B, and select line S. when S is 0,  $Y=A$  and  $S=1$ ,  $Y=B$

## Schematic and Symbol

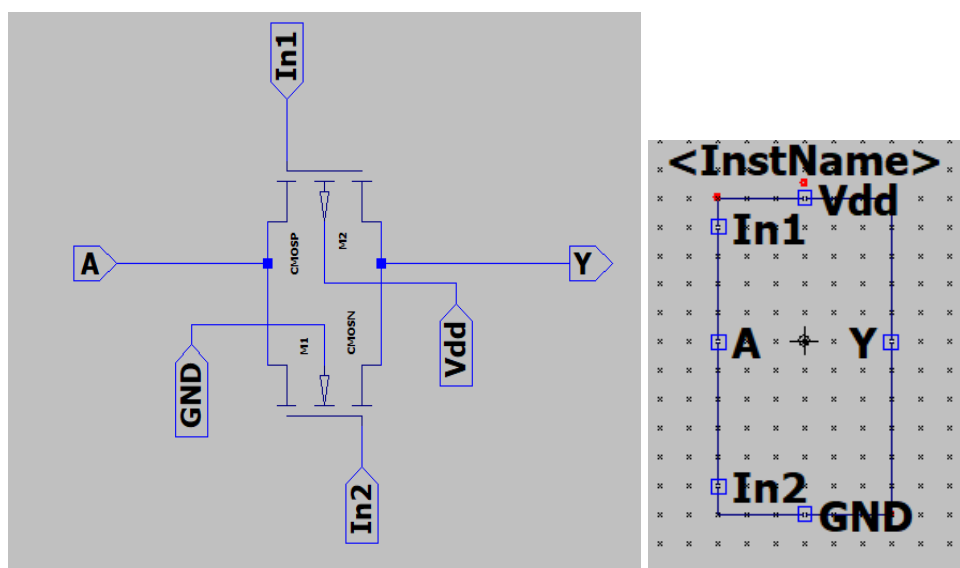
 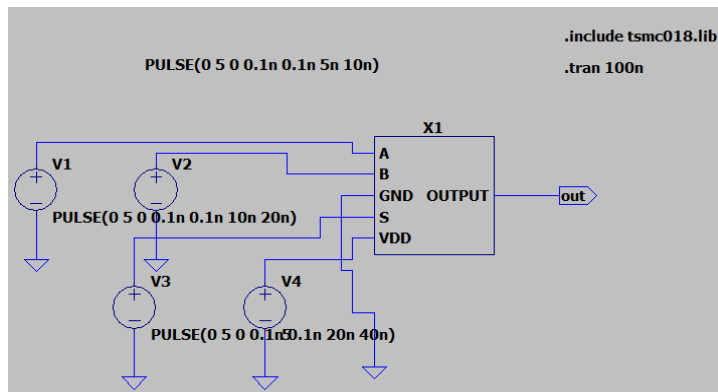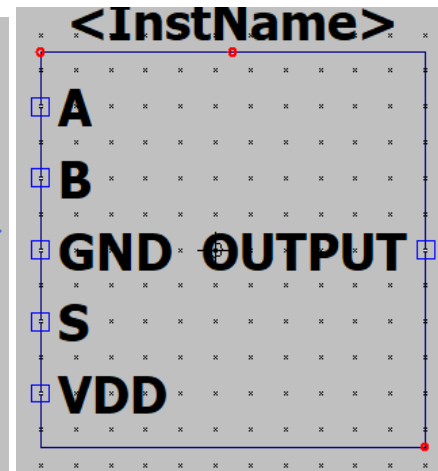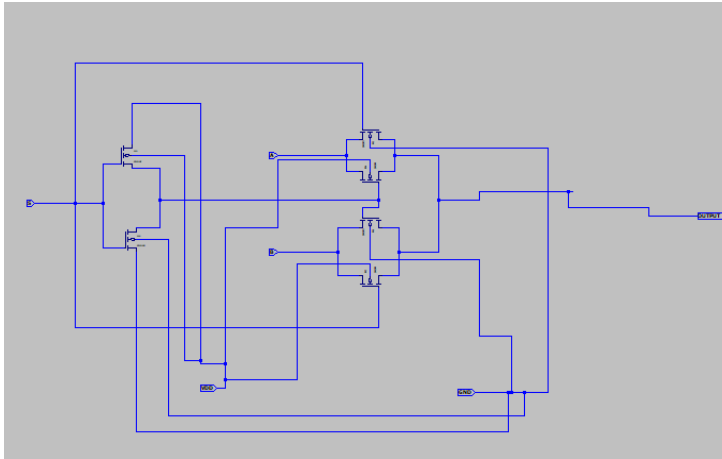
## 2:1 mux schematic symbol and test bench with graph



We have successfully implemented a 2:1mux using transmission gate



Power dissipation = 15.907  $\mu$ W

Number of cmos utilized = 6

Now we are going to realise 3 input full adder


But to implement it, first we design a 2 input xor gate using TG and then a 3 input xor gate which gives the sum expression and then we realise carry part of the full adder

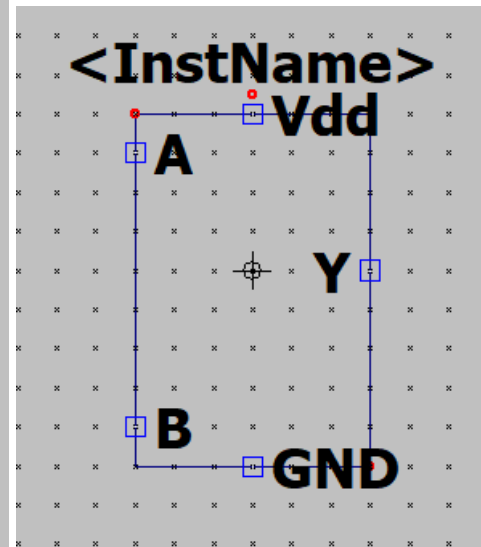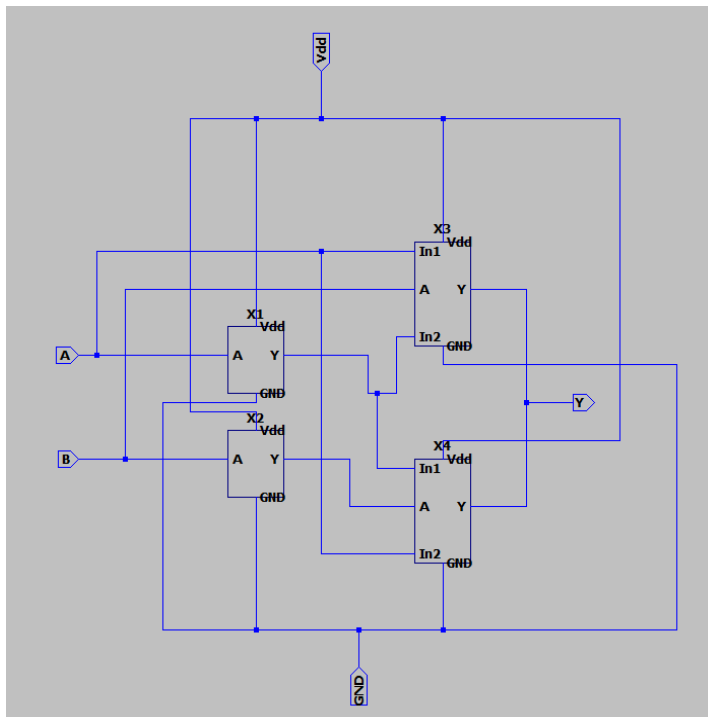
2 input XOR using TG schematic and symbol



2 input xor gate uses 8 cmos

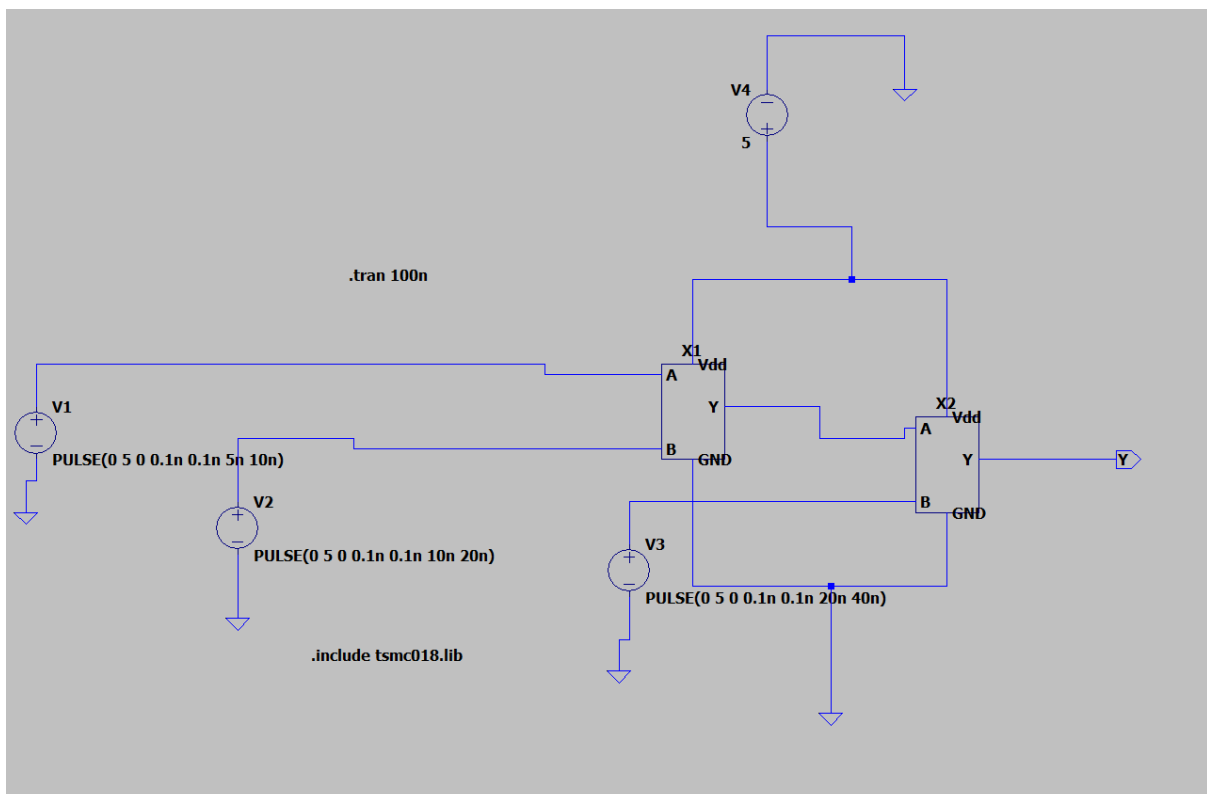3 input XOR gate schematic/testbench (SUM PART)



 

We have realised 3 input xor gate for each case possible

Truth table for verification



Inputs			Outputs	
A	B	C <sub>in</sub>	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Power dissipation =255.71uW

No of cmos used =16

Now we implement for the carry part of the full adder

Schematic/ testbench with graph

 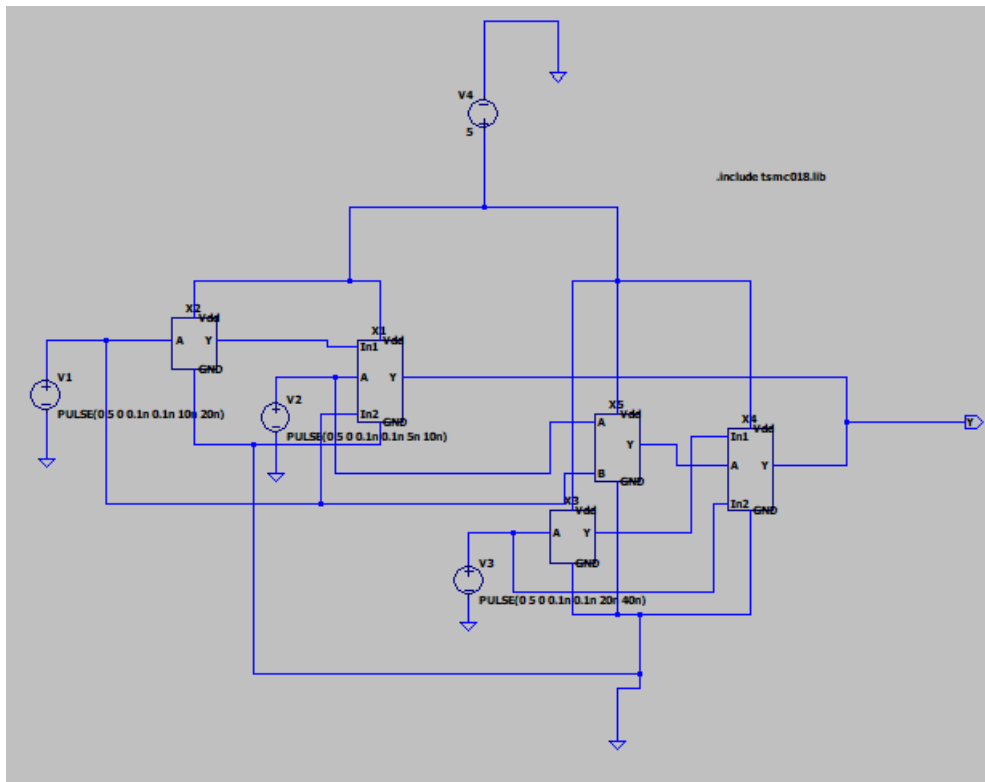

We can verify with each case.

Therefore, we have successfully implemented full adder using TG

Power dissipation =156.23uW

No of cmos used for carry part = 16

The number of cmos used in full adder while using TG circuit is lesser than when we try to realise a full adder using cmos directly

Result:

We have successfully designed and implemented 2:1 MUX,  
FULL ADDER