 


Calculation of delay :-

Equivalent CMOS circuit during high-to-low
Output transition



→ W.K.T.

current and v_{kg} are related in capacitor
is given by

$$i = C \frac{dv}{dt}$$

→ In a CMOS inverter

$$i_{D,p} - i_{D,n} = C_{load} \frac{dv_{out}}{dt}$$



→ In a high to low transition

$$v_{in} = V_{OH}$$

$$\therefore i_{D,p} = 0$$

$$\therefore C_{load} \frac{dv_{out}}{dt} = -i_{Dn}$$
  
$$dt = -C_{load} \int \frac{1}{i_{Dn}} dv_{out}$$



$$V_{ds} > V_{gs} - V_{Tn}$$

$$> \frac{V_{in} - V_{Th}}{V_{OH} - V_{Th}}$$

→ From t_0 to t_1 , nMOS is operating in saturation region

$$I_{D,n} = \frac{K_n}{2} (V_{in} - V_{tn})^2$$

$$= \frac{K_n}{2} [V_{OH} - V_{tn}]^2$$

$$\therefore \int_{t=t_0}^{t=t_1} dt = C_{load} \int_{V_0=V_{OH}}^{V_0=V_{OH}-V_{tn}} \left(\frac{1}{I_{Dn}} \right) dV_{out}$$

$$= -C_{load} \int_{V_0=V_{OH}}^{V_0=V_{OH}-V_{tn}} \frac{1}{\frac{K_n}{2} (V_{OH} - V_{tn})^2} dV_{out}$$

$$= -\frac{2C_{load}}{K_n (V_{OH} - V_{tn})^2} \int_{V_0=V_{OH}}^{V_0=V_{OH}-V_{tn}} dV_{out}$$

$$= -\frac{2C_{load}}{K_n (V_{OH} - V_{tn})^2} [V_{OH} - V_{OH} - V_{tn}]$$

$$= \frac{2C_{load} V_{tn}}{K_n (V_{OH} - V_{tn})^2}$$

@ $t = t' \quad \bar{L}_O \quad t = t_1$

$$\int_{t=t'}^{t=t_1} dt = -C_{load} \int_{V_{out}=V_{OH}-V_{tn}}^{V_{out}=V_{50\%}} \frac{1}{I_{On}} dV_{out}$$

→ In this region MOSFET Operating in Linear region

$$I_{dn} = \frac{1}{2} K_n \left[2(V_{in} - V_{tn}) V_{out} - V_{out}^2 \right]$$

$$= \frac{K_n}{2} \left[2(V_{OH} - V_{tn}) V_{out} - V_{out}^2 \right]$$

$$\int_{t=t'}^{t=t_1} dt = -C_{load} \int_{V_{out}=V_{OH}-V_{tn}}^{V_{out}=V_{50}} \frac{1}{\frac{K_n}{2} (2(V_{OH} - V_{tn}) V_{out} - V_{out}^2)} dV_{out}$$

$$= \frac{C_{load} 2}{K_n} \int_{V_{out}=V_{OH}-V_{tn}}^{V_{out}=V_{50}} \frac{1}{2(V_{OH} - V_{tn}) V_{out} - V_{out}^2} dV_{out}$$

$$\int \frac{1}{2\alpha x - x^2} dx = \int \frac{1}{2\alpha x - x^2 + \alpha^2 - \alpha^2} dx$$

$$= \int \frac{1}{\alpha^2 - (x - \alpha)^2} dx$$

$$\int \frac{1}{\alpha^2 - (x - \alpha)^2} dx = \frac{1}{2\alpha} \ln \left[1 + \frac{x}{\alpha} \right] - \ln \left[1 - \frac{x}{\alpha} \right] = \ln \left[\frac{x}{2\alpha - x} \right]$$

$\frac{1}{2\alpha} \ln \cdot \left(\frac{x}{2\alpha - x} \right)$

$$\int \frac{1}{\alpha^2 - (x - \alpha)^2} dx = \frac{1}{2(V_{OH} - V_{TN})} \cdot \ln \left[\frac{V_{out}}{2(V_{OH} - V_{TN}) - V_{out}} \right]$$

$V_{out} = V_{50}$

$$t_1 - t' = \frac{-2C_{load}}{2(V_{OH} - V_{TN})K_n} \cdot \ln \left[\frac{V_{out}}{2(V_{OH} - V_{TN}) - V_{out}} \right]$$

$V_{out} = V_{50}$
 $V_{out} = V_{OH} - V_{TN}$

$$= \frac{C_{load}}{(V_{OH} - V_{TN})K_n} \ln \left[\frac{2(V_{OH} - V_{TN}) - V_{out}}{V_{out}} \right]$$

$V_{out} = V_{50}$
 $V_{out} = V_{OH} - V_{TN}$

$$\frac{C_{load}}{(V_{OH} - V_{TN})K_n} \ln \left[\frac{2(V_{OH} - V_{TN}) - V_{50}}{V_{50}} \right]$$

D

$$- \ln \left[\frac{2(V_{OH} - V_{TN}) - (V_{OH} - V_{TN})}{V_{OH} - V_{TN}} \right]$$

$$= \frac{C_{load}}{K_n (V_{OH} - V_{TN})} \ln \left[\frac{2(V_{OH} - V_{TN}) - V_{50}}{V_{50}} \right]$$

$$\therefore \tau_{PHL} = \frac{2 C_{load} V_{TN}}{K_n (V_{OH} - V_{TN})^2} + \frac{C_{load}}{K_n (V_{OH} - V_{TN})} \ln \left[\frac{2(V_{OH} - V_{TN}) - V_{50}}{V_{50}} \right]$$

$$= \frac{C_{load}}{K_n (V_{OH} - V_{TN})} \left[\frac{2 V_{TN}}{V_{OH} - V_{TN}} + \ln \left[\frac{2(V_{OH} - V_{TN})}{V_{50}} - 1 \right] \right]$$

$$V_{50} = \frac{V_{OH} + V_{OL}}{2}$$

$$\therefore \tau_{PHL} = \frac{C_{load}}{K_n (V_{OH} - V_{TN})} \left[\frac{2 V_{TN}}{V_{OH} - V_{TN}} + \ln \left[\frac{4(V_{OH} - V_{TN})}{V_{OH} + V_{OL}} - 1 \right] \right]$$

→ For CMOS Inverter

$$V_{OH} = V_{DD}$$

$$V_{OL} = 0$$

$$\tau_{PHL} = \frac{C_{load}}{K_n (V_{DD} - V_{TN})} \left[\frac{2 V_{TN}}{V_{DD} - V_{TN}} + \ln \left(\frac{4(V_{DD} - V_{TN})}{V_{DD}} - 1 \right) \right]$$

→ when input voltage switches from V_{OH} to V_{OL}
 nMOS transistor cut-off

$$\tau_{PLH} = \frac{C_{load}}{K_p(V_{OH} - V_{OL} - |V_{TP}|)} \left[\frac{2|V_{TP}|}{V_{OH} - V_{OL} - |V_{TP}|} + \ln \left(\frac{2(V_{OH} - V_{OL} - |V_{TP}|)}{V_{OH} - V_{OL}} \right) \right]$$

$$V_{OH} = V_{DD}$$

$$V_{OL} = 0$$

$$\tau_{PLH} = \frac{C_{load}}{K_p(V_{DD} - |V_{TP}|)} \left[\frac{2|V_{TP}|}{V_{DD} - |V_{TP}|} + \ln \left[\frac{4(V_{DD} - |V_{TP}|)}{V_{DD}} - 1 \right] \right]$$

Comparing τ_{PHL} & τ_{PLH} equations


$$\tau_{PHL} = \tau_{PLH} \quad \text{If}$$

$$V_{T,n} = |V_{T,p}|$$

$$K_n = K_p$$

$$\frac{W_p}{W_n} = \frac{\mu_n}{\mu_p}$$

Inverter Design with delay Constraints

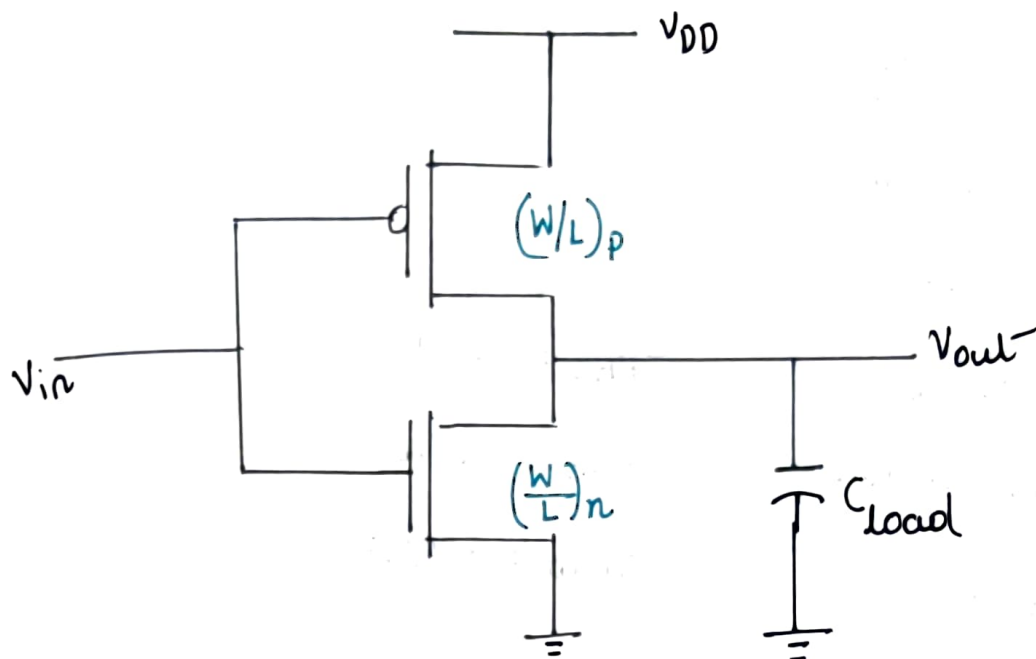

→ The goal is to determine channel dimensions of NMOS & PMOS transistors

→ Design constraints of CMOS transistors are

- Noise margin
- Silicon area
- Power dissipation
- Propagation delay

$$\left\{ \left(\frac{W}{L} \right)_n = \frac{C_{load}}{\tau_{PHL} \mu_n C_{ox} (V_{DD} - V_{Tn})} \cdot \left[\frac{2V_{Tn}}{V_{DD} - V_{Tn}} + \ln \left(\frac{4(V_{DD} - V_{Tn})}{V_{DD}} - 1 \right) \right] \right.$$

$$\left. \left(\frac{W}{L} \right)_p = \frac{C_{load}}{\tau_{PLH} \mu_p C_{ox} (V_{DD} - V_{Tp})} \cdot \left[\frac{2V_{Tp}}{V_{DD} - |V_{Tp}|} + \ln \left(\frac{4(V_{DD} - |V_{Tp}|)}{V_{DD}} - 1 \right) \right] \right\}$$

$$1. \mu_n C_{ox} = 120 \frac{\mu A}{V^2}$$

$$\mu_p C_{ox} = 60 \frac{\mu A}{V^2}$$

$$L = 0.6 \mu m$$

$$V_{T0n} = 0.8 V$$

$$V_{T0p} = -1 V$$

$$W_{min} = 1.2 \mu m$$

$$V_{TH} = 1.5 V$$

$$V_{DD} = 3 V$$

$$\tau_{PHL} = 0.2 ns$$

$$\tau_{PLH} = 0.15 ns$$

$$C_{load} = 300 fF$$


$$\left(\frac{W}{L}\right)_n = \frac{C_{load}}{\tau_{PHL} \mu_n C_{ox} (V_{DD} - V_{Tn})} \left[\frac{2 V_{Tn}}{V_{DD} - V_{Tn}} + \ln \left(\frac{4 (V_{DD} - V_{Tn})}{V_{DD}} \right) \right]$$

$$= \frac{300 \times 10^{-15}}{0.2 \times 10^{-9} \times 120 \times 10^{-6} (3 - 0.8)} \left[\frac{2 \times 0.8}{3 - 0.8} + \ln \left(\frac{4 (3 - 0.8)}{3} \right) \right]$$

$$= \underline{7.9}$$

$$\left(\frac{W}{L}\right)_p = \frac{C_{load}}{\tau_{PLH} \mu_p C_{ox} (V_{DD} - V_{Tp})} \left[\frac{2 V_{Tp}}{V_{DD} - V_{Tp}} + \ln \left(\frac{4 (V_{DD} - V_{Tp})}{V_{DD}} \right) \right]$$

$$= \underline{25.2}$$

 

$$t = 0.35 \text{ ns}$$

2 $\rightarrow 0.5 \text{ V} \rightarrow$ nMOS operates in Linear

$$t = \frac{C_{load}}{K_n (V_{DD} - V_{TOn})} \ln \left[\frac{2(V_{OH} - V_{TOn}) - V_{out}}{V_{out}} \right]^{0.5}$$

$$.35 \text{ ns} = \frac{300 \times 10^{-15}}{120 \times 10^{-6} \left(\frac{W}{L} \right)_n [3 - 0.8]} \left(\ln \left[\frac{2(3 - 0.8) - 0.5}{0.5} \right] - \ln \left[\frac{2(3 - 0.8) - 2}{2} \right] \right)$$


$$0.35 \times 10^{-9} = \frac{300 \times 10^{-15}}{120 \times 10^{-6} \left(\frac{W}{L} \right)_n 2.2} \left[\ln \left(\frac{3.9}{0.5} \right) - \ln \left(\frac{2.4}{2} \right) \right]$$

$$\left(\frac{W}{L} \right)_n = 6.1$$

$$V_{th} = \frac{V_{TOn} + \sqrt{\frac{1}{K_R}} (V_{DD} + V_{ToP})}{1 + \sqrt{\frac{1}{K_R}}} = 1.5 \quad K_R = 0.51$$

$$K_R = \frac{\mu_n C_{ox} \left(\frac{W}{L} \right)_n}{\mu_p C_{ox} \left(\frac{W}{L} \right)_p} = 0.51 \quad \left(\frac{W}{L} \right)_p = \underline{31}$$

CMOS Ring Oscillator

 

- Consider cascaded connection of three identical CMOS inverters
- Here o/p node of 3rd inverter acts as a input node of first inverter
- Here this configuration forms voltage feed back loop.
- A closed loop cascaded connection of any odd no of inverters display astable behaviour.
- \therefore circuit is called as ring Oscillator
- * T Oscillating period in terms of avg propagation delay is given by

$$T = \tau_{PHL1} + \tau_{PLH1} + \tau_{PHL2} + \tau_{PLH2} + \tau_{PHL3} + \tau_{PLH3}$$


$$= 2\tau_p + 2\tau_p + 2\tau_p$$

$$= 6\tau_p$$

$$= \underline{\underline{3 \cdot 2\tau_p}}$$

$$\rightarrow f = \frac{1}{T} = \frac{1}{2 \times n \times \tau_p}$$

$n = \underline{\underline{\text{no}}}$ of Inverter stages.

 

Problem 1.

1. consider a CMOS inverter with following spec

$$V_{DD} = 3.3$$

$$V_{GS} = 3.3V$$

$$I_{sat} = 2mA \quad \text{if } V_{DS} > 2.5V$$

input is a step input

calculate τ_{PHL}

$$C_L = 300fF.$$

$$dt = - \frac{C}{I_D} dV_{out}$$

$$\int_0^{t_{sat}} dt = - C \int_{3.3}^{2.5} \frac{1}{2.5} dV_{out}$$

$$= \frac{-300 \times 10^{-15}}{2.5mA} (-0.8)$$

$$= \underline{\underline{120ps}}$$

$$\int_{t_{sat}}^{t_{SD}} dt = - C \int_{2.5}^{1.65} \frac{1}{I_{Linear}} dV_{out}$$

$$= -C \int_{2.5}^{1.65} \frac{1}{\frac{K_n}{2} [2(V_{GS} - V_T) V_{ds} - V_{ds}^2]} dV_{out}$$

$$= -300 \times 10^{-15} \int_{2.5}^{1.65} \frac{1}{\frac{K_n}{2} [2(3.3 - 0.8) V_0 - V_0^2]} dV_{out}$$

$$I_{sat} = \frac{K_n}{2} (V_{GS} - V_{Tn})^2$$

$$2 \times 10^{-3} \times 2 = K_n [3.3 - 0.8]^2$$

$$K_n = \frac{4 \times 10^{-3}}{2.5^2}$$

$$= 0.64 \times 10^{-3}$$

$$= -300 \times 10^{-15} \int_{2.5}^{1.65} \frac{1}{\frac{0.64 \times 10^{-3}}{2} [5V_0 - V_0^2]} dV_{out}$$

$$= \frac{-300 \times 10^{-15} \times 2}{0.64 \times 10^{-3}} \ln \left[\frac{V_0}{5 - V_0} \right]_{2.5}^{1.65}$$

$$= \frac{-600 \times 10^{-15}}{0.64 \times 10^{-3}} \ln \left[\frac{1.65}{5 - 1.65} \right] - \ln \left[\frac{2.5}{5 - 2.5} \right]$$

$$= 133 \text{ PS}$$

$$t_{\text{delay}} = 120 + 133 = \underline{\underline{253 \text{ ps}}}$$

$$2) \quad V_{DD} = 5 \text{ V}$$

$$\tau_{\text{fall}} = ?$$

$$\mu_n C_{ox} = 20 \frac{\text{MA}}{\text{V}^2}$$

$$V_{out} = V_{q0} = 4.5 \text{ V}$$

$$\left(\frac{W}{L}\right)_n = 10$$

$$V_{out} = V_{10} = 0.5 \text{ V}$$

$$V_{Tn} = 1$$

$$C_L = 1 \text{ pF}$$

$$\tau = \frac{C \Delta V}{I_{\text{avg}}}$$

$$I_{\text{avg}} = \frac{1}{2} \left[\overset{90\%}{I_1} + \underset{10\%}{I_2} \right]$$

\uparrow Sat linear

Falling delay

$$V_{in} = 5 \text{ V}$$

$$V_{out} = (Sat) = 4.5$$

$$V_{out} (\text{Linear}) = 0.5$$



$$\frac{1}{2} \left[\frac{K_n}{2} [V_{in} - V_{Tn}]^2 + \frac{K_n}{2} [2(V_{in} - V_{Tn})V_{out} - V_{out}^2] \right]$$

$$= \frac{1}{2} \left[\frac{1}{2} 20 \times 10^{-6} \times 10 [5 - 1]^2 + \frac{1}{2} 20 \times 10^{-6} \times 10 [2(5 - 1)0.5 - 0.5^2] \right]$$

$$= \underline{\underline{0.9875 \text{ mA}}}$$

Switching power dissipation of CMOS Inverter

Circuit

 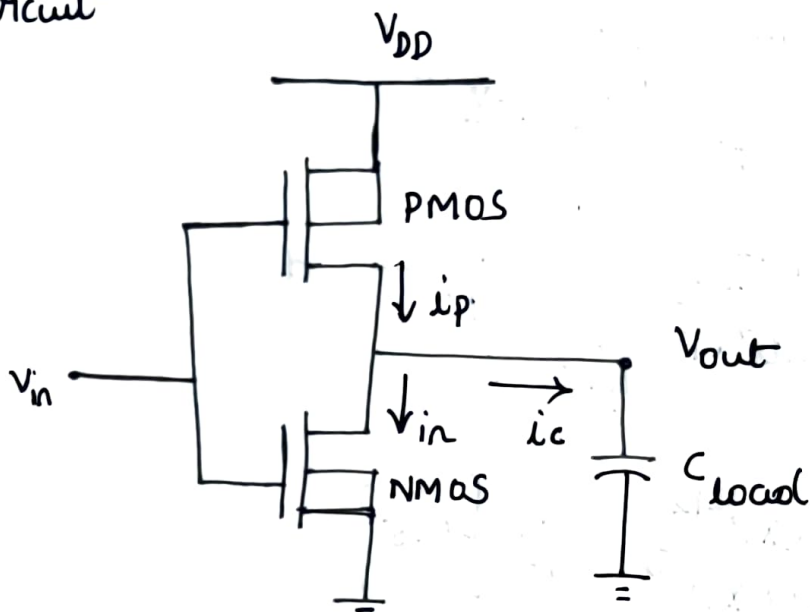

→ W.K.T. static power dissipation of CMOS inverter is negligible

→ When i/p Switches from logic 0 to logic 1 or logic 1 to logic 0 CMOS inverter inevitably dissipate power

→ Typical i/p and o/p waveforms (v_{tg} & current) shown in figure.

→ When i/p Switches from low to high PMOS off
NMOS on

→ In this phase C_{load} discharges through NMOS.

→ Thus i_c = instantaneous drain current of NMOS

→ When i/p Switches from high to Low PMOS on
NMOS off

→ In this phase C_{load} charges towards V_{DD}

i_c = instantaneous drain current of PMOS.

→ Avg power dissipation of CMOS inverter is given by

$$P_{avg} = \frac{1}{T} \int_0^T v(t) i(t) dt$$

$$= \frac{1}{T} \int_0^{T/2} v_c(t) i_c(t) dt + \int_{\frac{T}{2}}^T v_c(t) i_c(t) dt$$

$0 \rightarrow \frac{T}{2}$ $v_c(t) = v_{out}$

NMOS on $i_c(t) = -i_n(t)$

$$= -C_{load} \frac{dv_o}{dt}$$

$\frac{T}{2} \rightarrow T$

$$v_c(t) = v_{DD} - v_o$$

PMOS on $i_c(t) = C_{load} \frac{dv_o}{dt}$

$$= \frac{1}{T} \int_0^{T/2} -C_{load} v_o \frac{dv_o}{dt} dt + \int_{\frac{T}{2}}^T (v_{DD} - v_o) C_{load} \frac{dv_o}{dt} dt$$

$$= \frac{1}{T} \left[-\frac{C_{load}}{2} \int_0^{T/2} 2V_0 \frac{dV_0}{dt} dt + \int_{\frac{T}{2}}^T V_{DD} C_{load} \frac{dV_0}{dt} dt \right. \\ \left. + \int_{\frac{T}{2}}^T -\frac{C_{load}}{2} 2V_0 \frac{dV_0}{dt} dt \right]$$

$$= \frac{1}{T} \left[-\frac{C_{load}}{2} \int_0^{T/2} \frac{dV_0^2}{dt} dt + \int_{\frac{T}{2}}^T V_{DD} C_{load} \frac{dV_0}{dt} dt \right. \\ \left. - \frac{C_{load}}{2} \int_{\frac{T}{2}}^T \frac{dV_0^2}{dt} dt \right]$$

$$= \frac{1}{T} \left[\left. -\frac{C_{load}}{2} V_0^2 \right|_0^{T/2} + C_{load} V_{DD} V_0 \right|_{\frac{T}{2}}^T - \left. \frac{C_{load}}{2} V_0^2 \right|_{\frac{T}{2}}^T \right]$$

$$= \frac{1}{T} \left[\cancel{\frac{C_{load} V_{DD}^2}{2}} + (C_{load} V_{DD}^2 - 0) - \left(\cancel{\frac{C_{load} V_{DD}^2}{2}} - 0 \right) \right]$$

$$P = \frac{1}{T} C_{load} V_{DD}^2$$

$$P = C_{load} V_{DD}^2 f$$

- Average power dissipation of CMOS inverter is proportional to switching frequency.
- \therefore Low power advantage of CMOS circuit is less prominent in high speed circuits
- P_{avg} is independent of transistor sizing.

Power delay product

- Power delay product PDP is a fundamental parameter which is used for measuring quality and performance of CMOS process.
- PDP can be interpreted as Average energy required for gate to switch its o/p v_{eq} from high to low or low to high.
- In CMOS energy dissipated
 - i) by PMOS n/w while o/p load is charging from $0 \rightarrow V_{DD}$
 - ii) by NMOS n/w while load is discharging from $V_{DD} \rightarrow 0$

$$PDP = \text{Power} \times \text{Delay}$$

$$= e V^2 f \times T$$

$$\underline{\underline{C V^2}}$$

→ Since PDP is proportional to C_{load} & V_{DD} , both these parameters should be minimized to achieve better performance.

→ PDP can also be written as

$$PDP = 2 \tau_p \cdot P_{avg}$$




$$= \cancel{2} \left[\frac{\tau_{PHL} + \tau_{PLH}}{\cancel{2}} \right] C_{load} V_{DD}^2 f$$

$$= (\cancel{\tau_{PHL}} + \cancel{\tau_{PLH}}) C_{load} V_{DD}^2 \frac{1}{\cancel{\tau_{PHL}} + \cancel{\tau_{PLH}}}$$

$$\underline{\underline{PDP = C_{load} V_{DD}^2}}$$

calculation of interconnection delay.

RC Delay models.

   

→ Interconnect line could be modeled as lumped RC n/w if time of flight across the interconnection line is significantly shorter than signal rise/fall time

$$V_{out} = V_{DD} \left(1 - \exp \left(- \frac{t}{RC} \right) \right)$$

$$t = \tau_{PLH} \quad V_{out} = V_{50\%} = \frac{V_{OH} - V_{OL}}{2} = \frac{V_{DD}}{2}$$

$$\frac{V_{DD}}{2} = V_{DD} \left[1 - e^{-\frac{\tau_{PLH}}{RC}} \right]$$

$$e^{-\frac{\tau_{PLH}}{RC}} = 0.5$$


$$-\frac{\tau_{PLH}}{RC} = -0.69$$

$$\underline{\underline{\tau_{PLH} \simeq 0.69 RC}}$$

Elmore delay :-

→ consider RC network

 - i There are no resistor loops in a n/w.
- ii all cap are connected b/w node & ground.
- iii There is only one s/p node in a circuit.



→ Let P_i is the unique path from s/p node to node i $i = 1, 2, 3, \dots, N$

$$\rightarrow \text{Let } P_{ij} = P_i \cap P_j$$

= Common path

$$C_{Di} = \sum_{j=1}^N C_j \sum_{\substack{\text{for all} \\ k \in P_{ij}}} R_k$$

Total
 $N = \underline{\text{no}}$ of nodes

i = node where
 delay is calculated

$$\begin{aligned} \therefore Z_{D7} &= C_1 R_1 + C_2 R_1 + C_3 R_1 + C_4 R_1 + C_5 R_1 \\ &+ C_6 (R_1 + R_6) + C_7 (R_1 + R_6 + R_7) + C_8 (R_1 + R_6 + R_7) \\ &= \end{aligned}$$

@ node 5

$$\begin{aligned} Z_{D5} &= C_1 R_1 + C_2 (R_1 + R_2) + C_3 (R_1 + R_2) + C_4 (R_1 + R_2 + R_4) \\ &+ C_5 (R_1 + R_2 + R_4 + R_5) + C_6 R_1 + C_7 R_1 + C_8 R_1 \\ &= \end{aligned}$$

$$\textcircled{4} \quad V_{\text{Ton}} = 0.8 \text{ V}$$

$$V_{\text{Top}} = -1 \text{ V}$$

$$\mu_n C_{ox} = \frac{50 \mu\text{A}}{\text{V}^2}$$

$$\mu_p C_{ox} = \frac{20 \mu\text{A}}{\text{V}^2}$$

$$V_{DD} = 5 \text{ V}$$

$$L_n = L_p = 1 \mu\text{m}$$

$$C_{out} = 2 \text{ pF}$$

$$V_{th} = 2.2 \text{ V}$$

$$\tau_{rise} = 5 \text{ ns}$$

$$V_{OH} = V_{DD} = 5 \text{ V}$$

$$V_{OL} = 0$$

$$\tau_{rise} =$$